

Government polytechnic kendrapara



DEPARTMENT

OF

**ELECTRONICS AND TELECOMMUNICATION
ENGINEERING**

LECTURE NOTES

Semester : 3rd

Subject: ELECTRONICS MEASUREMENT & INSTRUMENTATION (TH-4)

Prepared by : Rabindra Kumar Satapathy,

(PTGF. Electronics & Telecommunication Engg.)

UNIT-1

Qualities of Measurement

Introduction:

The measurement of any quantity plays very important role not only in science but in all branches of engineering, medicine and in almost all the human day to day activities.

The technology of measurement is the base of advancement of science. The role of science and engineering is to discover the new phenomena, new relationships, the laws of nature and to apply these discoveries to human as well as other scientific needs. The science and engineering is also responsible for the design of new equipments. The operation, control and the maintenance of such equipments and the processes is also one of the important functions of the science and engineering branches. All these activities are based on the proper measurement and recording of physical, chemical, mechanical, optical and many other types of parameters.

The measurement of a given parameter or quantity is the act or result of a quantitative comparison between a predefined standard and an unknown quantity to be measured. The major problem with any measuring instrument is the error. Hence, it is necessary to select the appropriate measuring instrument and measurement procedure which minimizes the error. The measuring instrument should not affect the quantity to be measured.

An electronic instrument is the one which is based on electronic or electrical principles for its measurement function. The measurement of any electronic or electrical quantity or variable is termed as an electronic measurement.

Advantages of Electronic Measurement

The advantages of an electronic measurement are

1. Most of the quantities can be converted by transducers into the electrical or electronic signals.
2. An electrical or electronic signal can be amplified, filtered, multiplexed, sampled and measured.
3. The measurement can easily be obtained in or converted into digital form for automatic analysis and recording.
4. The measured signals can be transmitted over long distances with the help of cables or radio links, without any loss of information.
5. Many measurements can be carried either simultaneously or in rapid succession.
6. Electronic circuits can detect and amplify very weak signals and can measure the events of very short duration as well.
7. Electronic measurement makes possible to build analog and digital signals. The digital signals are very much required in computers. The modern development in science and technology are totally based on computers.

Higher sensitivity, low power consumption and a higher degree of reliability are the important features of electronic instruments and measurements. But, for any measurement, a well defined set of standards and calibration units is essential. This chapter provides an introduction to different types of errors in measurement, the characteristics of an instrument and different calibration standards.

The **necessary requirements** for any measuring instrument are:

With the introduction of the instrument in the circuit, the circuit conditions should not be altered. Thus the quantity to be measured should not get affected due to the instrument used.

The power consumed by the instruments for their operation should be as small as possible.

Classification of Measuring Instruments:

1. Indicating Instruments
2. Recording Instruments
3. Integrating Instruments

Indicating Instruments: These instruments make use of a dial and pointer for showing or indicating magnitude of unknown quantity .ex: Voltmeter

Recording Instruments: These instruments give a continuous record of the given electrical quantity which is being measured over specific period.

Integrating Instruments: These instruments measure the total quantity of electricity delivered over period of time.

Performance Characteristics:

The performance characteristics of an instrument of an instrument are mainly divided in two types.

Static characteristics

Dynamic characteristics

Calibration: It is the process of making an adjustment or making a scale so that the readings of an instrument agree with the accepted and certified standard.

Static characteristics:

As mentioned earlier, the static characteristics are defined for the instruments which measure the quantities which do not vary with time. The various static characteristics are accuracy, precision, resolution, error, sensitivity, threshold, reproducibility, zero drift, stability and linearity.

Accuracy:

It is the degree of closeness with which the instrument reading approaches the true value of the quantity to be measured. It denotes the extent to which we approach the actual value of the quantity. It indicates the ability of instrument to indicate the true value of the quantity. The accuracy can be expressed in the following ways. Accuracy as 'Percentage of Full Scale Reading .

For example, the accuracy of an instrument having full scale reading of 50 units may be expressed as $\pm 0.1\%$ of full scale reading. From this accuracy indication, practically accuracy is expressed in terms of limits of error. So for the accuracy limits specified above, there will be ± 0.05 units error in any measurement. So for a reading of 50 units, there will be error of ± 0.05 units i.e. $\pm 0.1\%$ while for a reading of 25 units, there will be error of ± 0.05 units in the reading i.e. $\pm 0.2\%$. Thus as reading decreases, error in measurement is ± 0.05 units but net percentage error is more. Hence, specification of accuracy in this manner is highly misleading.

Accuracy as 'Percentage of True Value' : This is the best method of specifying the accuracy. It is to be specified in terms of the true value of quantity being measured. For example, it can be specified as $\pm 0.1\%$ of true value. This indicates that in such cases, as readings get smaller, error also gets reduced. Hence accuracy of the instrument is better than the instrument for which it is specified as percent of full scale reading.

Precision:

It is the measure of consistency or repeatability of measurements.

Let us see the basic difference between accuracy and precision. Consider an instrument on which, readings up to 1/1000th of unit can be measured. But the instrument has large zero adjustment error. Now every time reading is taken, it can be taken down upto 1/1000th of unit. So as the readings agree with each other, we say that the instrument is highly precise. But, though the readings are precise up to 1/1000th of unit, the readings are inaccurate due to large zero adjustment error. Every reading will be inaccurate, due to such error. Thus a precise instrument may not be accurate. Thus the precision means sharply or clearly defined and the readings agree among themselves. But there is no guarantee that readings are accurate. An instrument having zero error, if calibrated properly, can give accurate readings but in that case still, the readings can be obtained down upto 1/10th of unit only. Thus accuracy can be improved by calibration but not the precision of the instrument.

The precision is composed of two characteristics:

Conformity and

Number of significant figures.

Conformity:

Consider a resistor having true value as 2385692.0Ω , which is being measured by an ohmmeter. Now, the meter is consistently measuring the true value of the resistor. But the reader, can read consistently, a value as $2.4\text{ M}\Omega$ due to non availability of proper scale. The value $2.4\text{ M}\Omega$ is estimated by the reader from the available scale. There are no deviations from the observed value. The error created due to the limitation of the scale reading is a precision error.

Significant Figures:

The precision of the measurement is obtained from the number of significant figures, in which the reading is expressed. The significant figures convey the actual information about the magnitude and the measurement precision of the quantity.

Resolution:

It is the smallest increment of quantity being measured which can be detected with certainty by an instrument.

So if a nonzero input quantity is slowly increased, output reading will not increase until some minimum change in the input takes place. This minimum change which causes the change in the output is called resolution. The resolution of an instrument is also referred to as discrimination of the instrument. The resolution can affect the accuracy of the measurement.

Static Error:

The difference between the true value, A_t of the quantity that does not vary with respect to time and the indicated value of an instrument, A_i is known as **static error**, e_s . Mathematically, it can be represented as:

$$e_s = A_t - A_i$$

The term, static error signifies the inaccuracy of the instrument. If the static error is represented in terms of percentage, then it is called **percentage of static error**. Mathematically, it can be represented as:

$$\% e_s = \frac{e_s}{A_t} \times 100$$

Substitute, the value of e_s in the right hand side of above equation:

$$\% e_s = \frac{A_t - A_i}{A_t} \times 100$$

Where,

$\% e_s$ is the percentage of static error.

Sensitivity:

The sensitivity is always expressed by the manufacturers as the ratio of the magnitude of quantity being measured to the magnitude of the response. Actually, this definition is the reciprocal of the sensitivity is called inverse sensitivity or deflection factor. But manufacturers call this inverse sensitivity as sensitivity.

Inverse sensitivity = Deflection factor

Deflection factor = 1/ sensitivity = 1/S

The units of the sensitivity are millimeter per micro-ampere, millimeter per ohm, counts per volt,

Drift : Gradual shift in the measured value ,over an extended period, when there is no change in input.

Threshold: The minimum value of input for which the device just starts to respond.

Range/Span: The minimum and maximum value of quantity so that the device is capable of measuring.

Repeatability: A measure of how well the output returns to a given value when the same precise input is applied several times. Or The ability of an instrument to reproduce a certain set of reading within a given accuracy.


Linearity: Input output relationship of a device must be linear.

But practical systems shows small deviations from the linear shape (allowed within the specified limits)

Hysteresis: Input is increased from negative value, output increases as indicated by curve 1

• Then the input is steadily decreased , output does not follow the same path , but lag by a certain value as indicated by curve 2 •

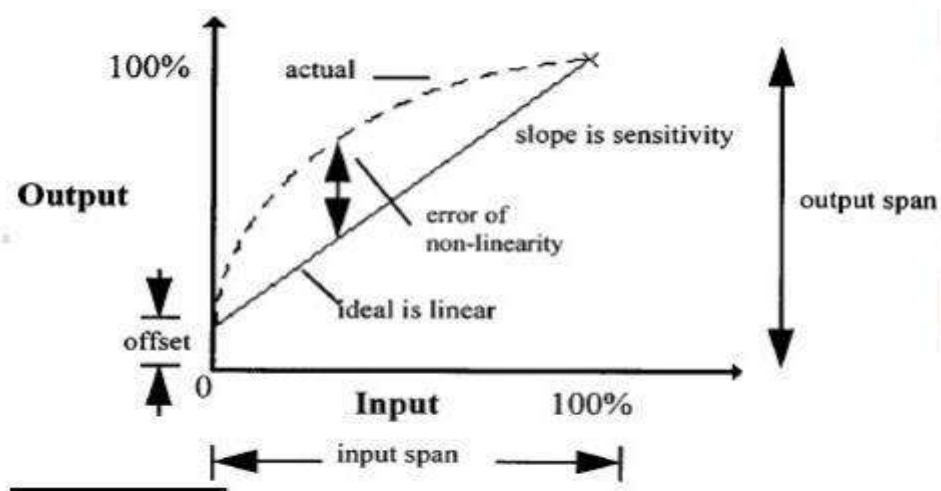The difference between the two curves is called Hysteresis.



DYNAMIC CHARACTERISTICS:

The response of instruments or systems to dynamic I/P s are also functions of time.

Instruments rarely respond instantaneously to changes in the measured variables.


Instead, they exhibit slowness or sluggishness due to such things as mass, thermal capacitance, fluid capacitance or electric capacitance.

• **Speed of Response:** It is the ability of a system to respond to sudden changes in the input signal/quantity

• **Fidelity:** It is the degree to which an instrument indicates the changes in the measured variable without dynamic error (Indication of how much faithfully system responds to the changes in input).

Lag: It is the retardation or delay in the response of an instrument to changes in the measured variable. Two types: Process lag(process) and Control lag (Instrument)

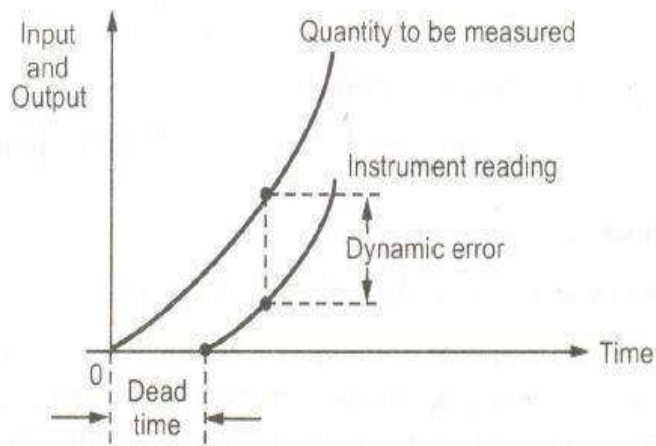Dynamic error:It is the difference between the true value of the variable to be measured, changing with time and the value indicated by the measurement system, assuming zero static error. The Fig. 1.13 shows the dead time, i.e. time delay and the dynamic error.



Types of errors:

The static error is defined earlier as the difference between the true value of the variable and the value indicated by the instrument. The static error may arise due to number of reasons. The static errors are classified as:

- Gross errors
- Systematic errors
- Random errors

Gross errors:

The gross errors mainly occur due to carelessness or lack of experience of a human being. These cover human mistakes in readings, recordings and calculating results. These errors also occur due to incorrect adjustments of instruments. These errors cannot be treated mathematically. These errors are also called personal errors. Some gross errors are easily detected while others are very difficult to detect.

The complete elimination of gross errors is not possible, but one can minimize them. Some errors are easily detected while others may be elusive. One of the basic gross errors that occur frequently is the improper use of an instrument. The error can be minimized by taking proper care in reading and recording the measurement parameter.

Systematic errors:

The systematic errors are mainly resulting due to the shortcomings of the instrument and the characteristics of the material used in the instrument, such as defective or worn parts, ageing effects, environmental effects, etc.

A constant uniform deviation of the operation of an instrument is known as a systematic error. There are three types of systematic errors as

- 1) Instrumental errors
- 2) Environmental errors
- 3) Observational errors

Instrumental errors :

These errors are mainly due to following three reasons

- Short-comings of instrument

These are because of the mechanical structure of the instruments eg. Friction in the bearings of various moving parts, irregular spring tensions, hysteresis, gear backlash, variation in air gap etc.

Misuse of instrument A good instrument if used in abnormal way gives misleading results. Poor initial adjustments, Improper zero setting, Using leads of high resistance. Elimination: Use the instrument intelligently & Correctly

- Loading effects Loading effects due to Improper way of using the instrument

- **Elimination.**

- Selecting proper instrument and the transducer for the measurement.

- Recognize the effect of such errors and apply the proper correction factors.

- Calibrate the instrument carefully against standard.

Environmental Errors (due to the External Conditions)

- The various factors : Temperature changes, Pressure, vibrations, Thermal emf., stray capacitance, cross capacitance, effect of External fields, Aging of equipments and Frequency sensitivity of an instrument.

Elimination • Using proper correction factors and using the instrument Catalogue • Using Temperature & Pressure control methods etc. • Reducing the effect of dust, humidity on the components in the instruments. • The effects of external fields can be minimized by using the magnetic or electrostatic shields of screens.

Observational Errors:

Observational errors are errors introduced by the observer. The most common error is the parallax error introduced in reading a meter scale, and the error of estimation when obtaining a reading from a meter scale. These errors are caused by the habits of individual observers. For example, an observer may always introduce an error by consistently holding his head too far to the left while reading a needle and scale reading.

In general, systematic errors can also be subdivided into static and dynamic errors. Static errors are caused by limitations of the measuring device or the physical laws governing its behavior. Dynamic errors are caused by the instrument not responding fast enough to follow the changes in a measured variable

Random errors:

Some errors still result, though the systematic and instrumental errors are reduced or at least accounted for. The causes of such errors are unknown and hence, the errors are called **random** errors. These errors cannot be determined in the ordinary process of taking the measurements.

These are errors that remain after gross and systematic errors have been substantially reduced or at least accounted for. Random errors are generally an accumulation of a large number of small effects and may be of real concern only in measurements requiring a high degree of accuracy. Such errors can be analyzed statistically.

These errors are due to unknown causes, not determinable in the ordinary process of making measurements. Such errors are normally small and follow the laws of probability. Random errors can thus be treated mathematically.

Absolute and relative errors:

When the error is specified in terms of an absolute quantity and not as a percentage, then it is called an absolute error.

Thus the voltage of 10 ± 0.5 V indicated ± 0.5 V as an absolute error. When the error is expressed as a percentage or as a fraction of the total quantity to be measured, then it is called relative error.

Limiting errors:

The manufacturers specify the accuracy of the instruments within a certain percentage of full scale reading. The components like the resistor, inductor, capacitor are guaranteed to be within a certain percentage of rated value. This percentage indicates the deviations from the nominal or specified value of the particular quantity. These deviations from the specified value are called **Limiting Errors**. These are also called **Guarantee Errors**.

Thus the actual value with the limiting error can be expressed

$$\text{mathematically as, } A_a = A_s \pm \Delta A$$

Where A_a = Actual value

A_s = Specified or rated

value ΔA = limiting error

or tolerance

Relative limiting error: This is also called fractional error. It is the ratio of the error to the specified magnitude of a quantity.

SOURCES OF ERROR


The sources of error, other than the inability of a piece of hardware to provide a true measurement, are as follows:

1. Insufficient knowledge of process parameters and design conditions
2. Poor design
3. Change in process parameters, irregularities, upsets, etc.
4. Poor maintenance
5. Errors caused by person operating the instrument or equipment
6. Certain design limitations

MEASURING INSTRUMENTS

Definition of instruments

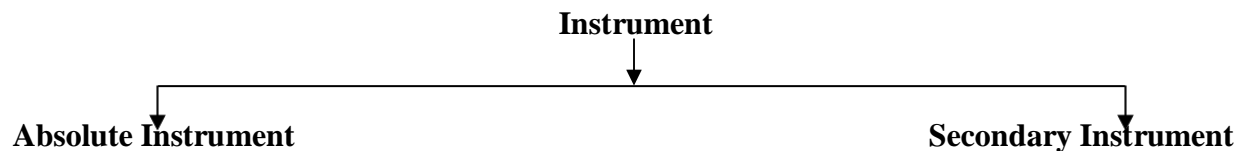An instrument is a device in which we can determine the magnitude or value of the quantity to be measured. The measuring quantity can be voltage, current, power and energy etc. Generally instruments are classified in to two categories.




Absolute instrument

An absolute instrument determines the magnitude of the quantity to be measured in terms of the instrument parameter. This instrument is really used, because each time the value of the measuring quantities varies. So we have to calculate the magnitude of the measuring quantity, analytically which is time consuming. These types of instruments are suitable for laboratory use. Example: Tangent galvanometer.

Secondary instrument

This instrument determines the value of the quantity to be measured directly. Generally these instruments are calibrated by comparing with another standard secondary instrument.

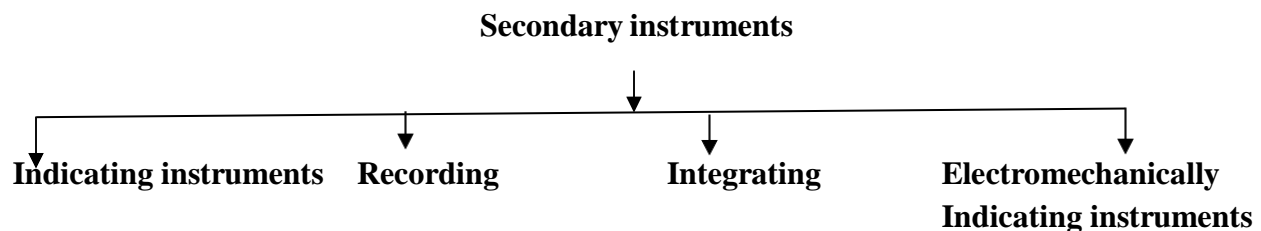Examples of such instruments are voltmeter, ammeter and wattmeter etc. Practically secondary instruments are suitable for measurement.



Indicating instrument

This instrument uses a dial and pointer to determine the value of measuring quantity. The pointer indication gives the magnitude of measuring quantity.

Recording instrument

This type of instruments records the magnitude of the quantity to be measured continuously over a specified period of time.

Integrating instrument

This type of instrument gives the total amount of the quantity to be measured over a specified period of time.

Electromechanical indicating instrument

For satisfactory operation electromechanical indicating instrument, three forces are necessary.

They are

- (a) Deflecting force
- (b) Controlling force
- (c) Damping force

Deflecting force

When there is no input signal to the instrument, the pointer will be at its zero position. To deflect the pointer from its zero position, a force is necessary which is known as deflecting force. A system which produces the deflecting force is known as a deflecting system. Generally a deflecting system converts an electrical signal to a mechanical force.

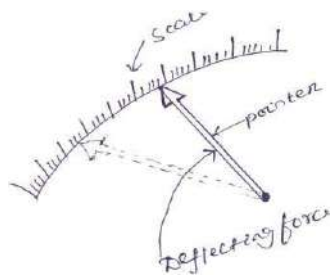


Fig. 1.1 Pointer scale

Magnitude effect

When a current passes through the coil (Fig.1.2), it produces an imaginary bar magnet. When a soft-iron piece is brought near this coil, it is magnetized. Depending upon the current direction, the poles are produced in such a way that there will be a force of attraction between the coil and the soft iron piece. This principle is used in moving iron attraction type instrument.

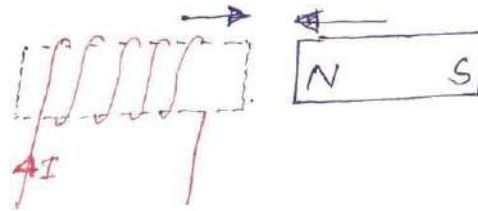


Fig. 1.2

If two soft iron pieces are placed near a current-carrying coil, there will be a force of repulsion between the two soft iron pieces. This principle is utilized in the moving iron repulsion type instrument.

Force between a permanent magnet and a current-carrying coil

When a current-carrying coil is placed under the influence of a magnetic field produced by a permanent magnet, a force is produced between them. This principle is utilized in the moving coil type instrument.

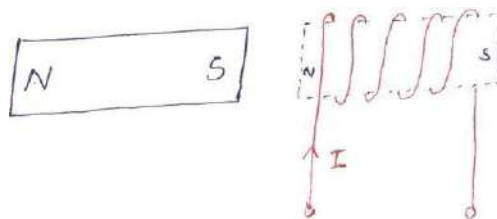


Fig. 1.3

Force between two current-carrying coils

When two current-carrying coils are placed closer to each other, there will be a force of repulsion between them. If one coil is movable and the other is fixed, the movable coil will move away from the fixed one. This principle is utilized in electro-dynamometer type instrument.

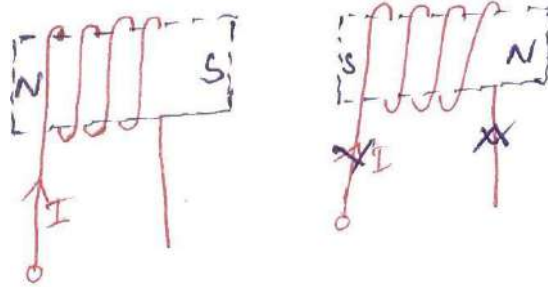


Fig. 1.4

Controlling force

To make the measurement indicated by the pointer definite (constant) a force is necessary which will be acting in the opposite direction to the deflecting force. This force is known as controlling force. A system which produces this force is known as a controlled system. When the external signal to be measured by the instrument is removed, the pointer should return back to the zero position. This is possibly due to the controlling force and the pointer will be indicating a steady value when the deflecting torque is equal to controlling torque.

$$T_d = T_c \quad (1.1)$$

Spring control

Two springs are attached on either end of spindle (Fig. 1.5). The spindle is placed in jewelled bearing, so that the frictional force between the pivot and spindle will be minimum. Two springs are provided in opposite direction to compensate the temperature error. The spring is made of phosphorous bronze.

When a current is supply, the pointer deflects due to rotation of the spindle. While spindle is rotate, the spring attached with the spindle will oppose the movements of the pointer. The torque produced by the spring is directly proportional to the pointer deflection θ .

$$T_C \propto \theta \quad (1.2)$$

The deflecting torque produced T_d proportional to 'I'. When $T_C = T_d$, the pointer will come to a steady position. Therefore

$$\theta \propto I \quad (1.3)$$

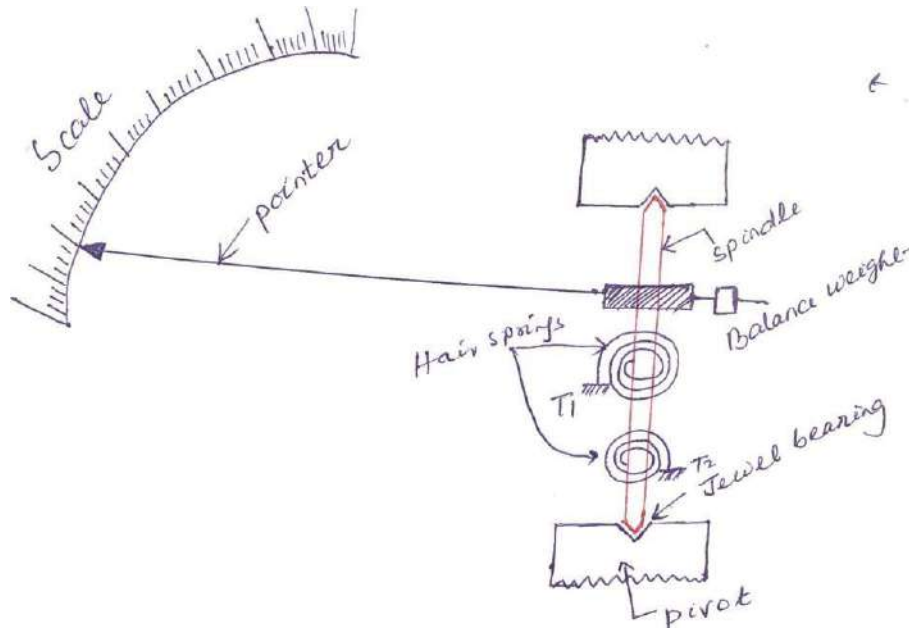


Fig. 1.5

Since, θ and I are directly proportional to the scale of such instrument which uses spring controlled is uniform.

Damping force

The deflection torque and controlling torque produced by systems are electro mechanical. Due to inertia produced by this system, the pointer oscillates about its final steady position before coming to rest. The time required to take the measurement is more. To damp out the oscillation quickly, a damping force is necessary. This force is produced by different systems.

- (a) Air friction damping
- (b) Fluid friction damping
- (c) Eddy current damping

Air friction damping

The piston is mechanically connected to a spindle through the connecting rod (Fig. 1.6). The pointer is fixed to the spindle moves over a calibrated dial. When the pointer oscillates in clockwise direction, the piston goes inside and the cylinder gets compressed. The air pushes the piston upwards and the pointer tends to move in anticlockwise direction.

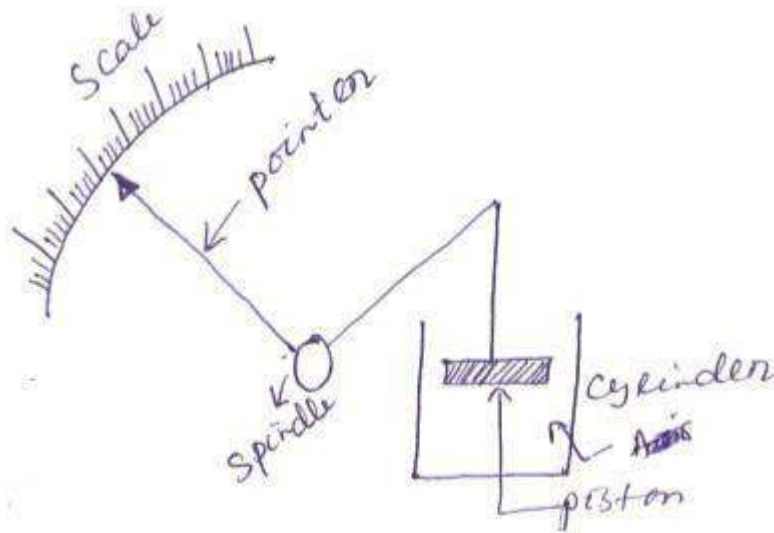


Fig. 1.6

If the pointer oscillates in anticlockwise direction the piston moves away and the pressure of the air inside cylinder gets reduced. The external pressure is more than that of the internal pressure. Therefore the piston moves down wards. The pointer tends to move in clock wise direction.

Eddy current damping

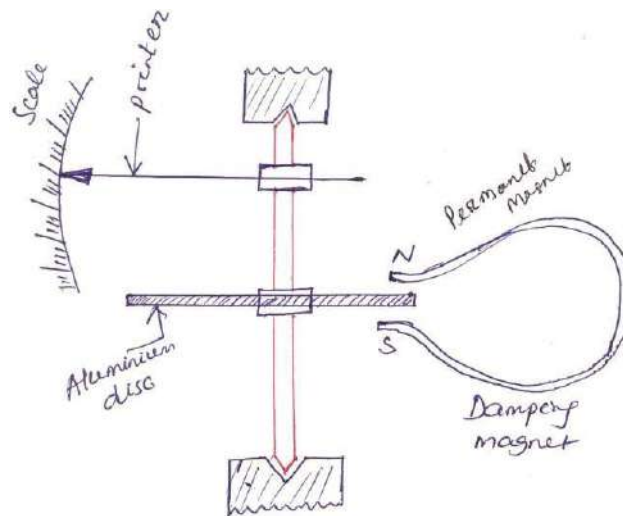


Fig. 1.6 Disc type

An aluminum circular disc is fixed to the spindle (Fig. 1.6). This disc is made to move in the magnetic field produced by a permanent magnet.

When the disc oscillates it cuts the magnetic flux produced by damping magnet. An emf is induced in the circular disc by Faraday's law. Eddy currents are established in the disc since it has several closed paths. By Lenz's law, the current carrying disc produces a force in a direction opposite to oscillating force. The damping force can be varied by varying the projection of the magnet over the circular disc.

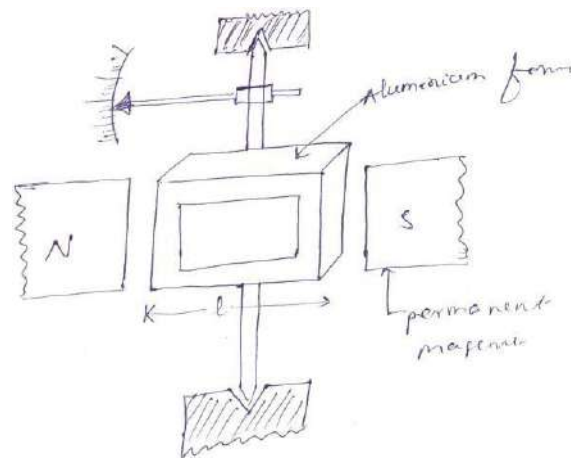


Fig. 1.6 Rectangular type

Permanent Magnet Moving Coil (PMMC) instrument

One of the most accurate type of instrument used for D.C. measurements is PMMC instrument.

Construction: A permanent magnet is used in this type instrument. Aluminum former is provided in the cylindrical in between two poles of the permanent magnet (Fig. 1.7). Coils are wound on the aluminum former which is connected with the spindle. This spindle is supported with jeweled bearing. Two springs are attached on either end of the spindle. The terminals of the moving coils are connected to the spring. Therefore the current flows through spring 1, moving coil and spring 2.

Damping: Eddy current damping is used. This is produced by aluminum former.

Control: Spring control is used.

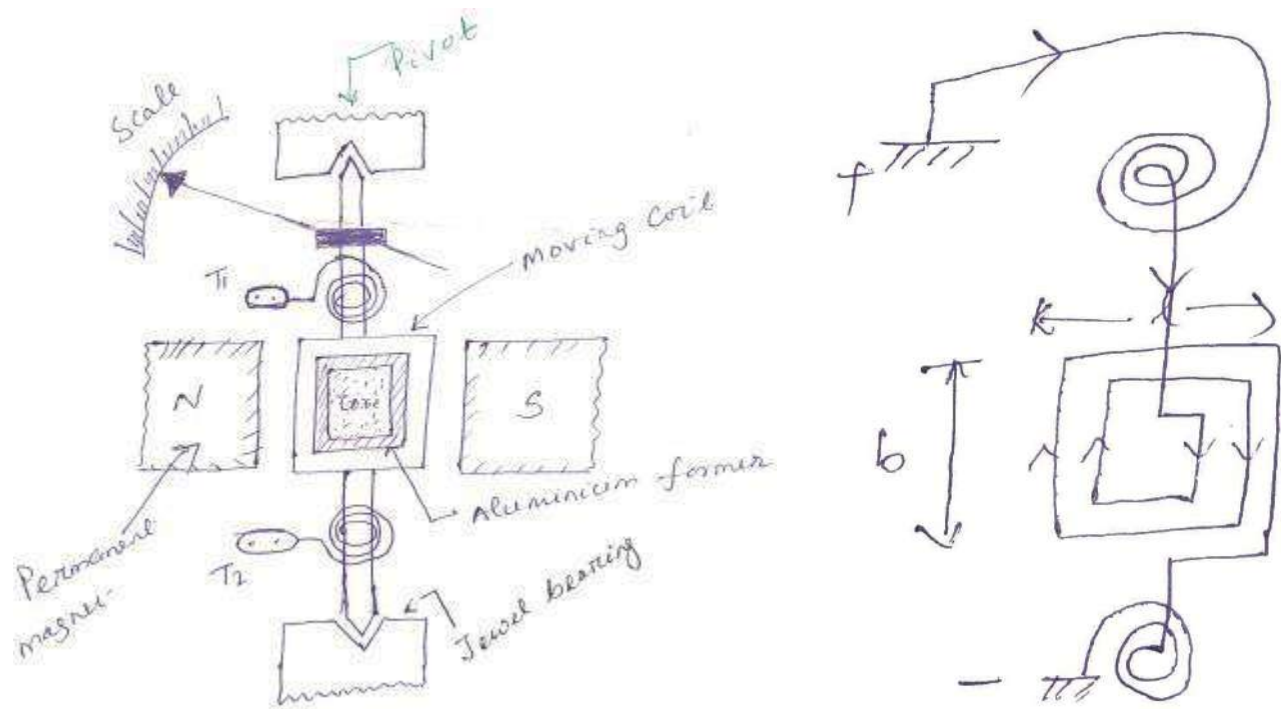


Fig. 1.7

Principle of operation

When D.C. supply is given to the moving coil, D.C. current flows through it. When the current carrying coil is kept in the magnetic field, it experiences a force. This force produces a torque and the former rotates. The pointer is attached with the spindle. When the former rotates, the pointer moves over the calibrated scale. When the polarity is reversed a torque is produced in the opposite direction. The mechanical stopper does not allow the deflection in the opposite direction. Therefore the polarity should be maintained with PMMC instrument.

If A.C. is supplied, a reversing torque is produced. This cannot produce a continuous deflection. Therefore this instrument cannot be used in A.C.

Torque developed by PMMC

- Let T_d =deflecting torque
- T_C = controlling torque
- θ = angle of deflection
- K=spring constant
- b=width of the coil

l =height of the coil or length of coil

N =No. of turns

I =current

B =Flux density

A =area of the coil

The force produced in the coil is given by

$$F = BIL \sin \theta \quad (1.4)$$

When $\theta = 90^\circ$

$$\text{For } N \text{ turns, } F = NBIL \quad (1.5)$$

$$\text{Torque produced } T_d = F \times \perp_r \text{ distance} \quad (1.6)$$

$$T_d = NBIL \times b = BINA \quad (1.7)$$

$$T_d = BAN I$$

$$T_d \propto I$$

Advantages

- ✓ Torque/weight is high
- ✓ Power consumption is less
- ✓ Scale is uniform
- ✓ Damping is very effective
- ✓ Since operating field is very strong, the effect of stray field is negligible
- ✓ Range of instrument can be extended

Disadvantages

- ✓ Use only for D.C.
- ✓ Cost is high
- ✓ Error is produced due to ageing effect of PMMC
- ✓ Friction and temperature error are present

Moving Iron (MI) instruments

One of the most accurate instrument used for both AC and DC measurement is moving iron instrument. There are two types of moving iron instrument.

- Attraction type
- Repulsion type

Attraction type M.I. instrument

Construction: The moving iron fixed to the spindle is kept near the hollow fixed coil (Fig. 1.10). The pointer and balance weight are attached to the spindle, which is supported with jeweled bearing. Here air friction damping is used.

Principle of operation

The current to be measured is passed through the fixed coil. As the current is flow through the fixed coil, a magnetic field is produced. By magnetic induction the moving iron gets magnetized. The north pole of moving coil is attracted by the south pole of fixed coil. Thus the deflecting force is produced due to force of attraction. Since the moving iron is attached with the spindle, the spindle rotates and the pointer moves over the calibrated scale. But the force of attraction depends on the current flowing through the coil.

Torque developed by M.I

Let 'θ' be the deflection corresponding to a current of 'i' amp

Let the current increases by di , the corresponding deflection is 'θ + $d\theta$ '

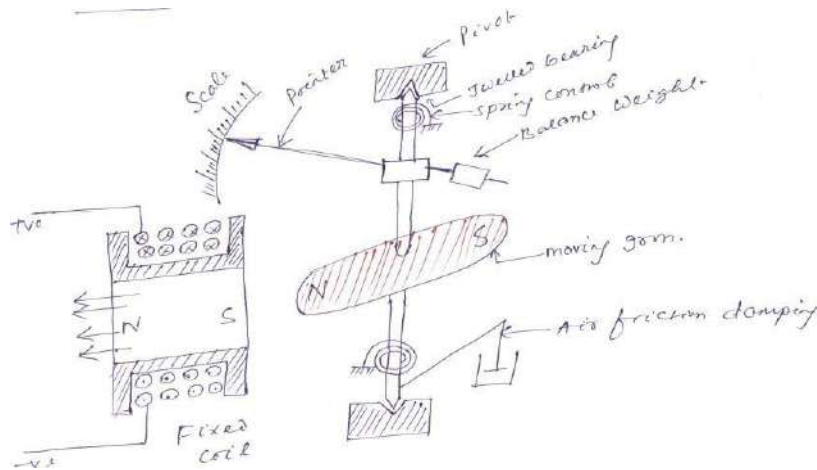


Fig. 1.10

There is change in inductance since the position of moving iron change w.r.t the fixed electromagnets.

Let the new inductance value be ' $L+dL$ '. The current change by ' di ' is dt seconds.

Let the emf induced in the coil be ' e ' volt.

$$e = \frac{d}{dt}(Li) = L \frac{di}{dt} + i \frac{dL}{dt} \quad (1.22)$$

Multiplying by ' idt ' in equation (1.22)

$$e \times idt = L \frac{di}{dt} \times idt + i \frac{dL}{dt} \times idt \quad (1.23)$$

$$e \times idt = Lidi + i^2 dL \quad (1.24)$$

Eqⁿ (1.24) gives the energy is used in to two forms. Part of energy is stored in the inductance.

Remaining energy is converted in to mechanical energy which produces deflection.

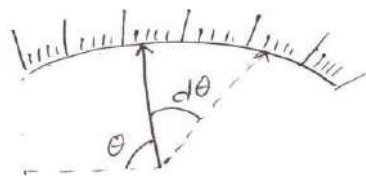
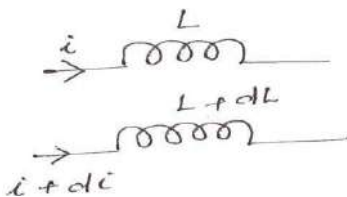


Fig. 1.11

Change in energy stored=Final energy-initial energy stored

$$\begin{aligned}
 &= \frac{1}{2}(L + dL)(i + di)^2 - \frac{1}{2}Li^2 \\
 &= \frac{1}{2}\{(L + dL)(i^2 + di^2 + 2idi) - Li^2\} \\
 &= \frac{1}{2}\{(L + dL)(i^2 + 2idi) - Li^2\} \\
 &= \frac{1}{2}\{Li^2 + 2Lidi + i^2dL + 2ididL - Li^2\} \\
 &= \frac{1}{2}\{2Lidi + i^2dL\} \\
 &= Lidi + \frac{1}{2}i^2dL
 \end{aligned} \tag{1.25}$$

Mechanical work to move the pointer by $d\theta$

$$= T_d d\theta \tag{1.26}$$

By law of conservation of energy,

Electrical energy supplied=Increase in stored energy+ mechanical work done.

Input energy= Energy stored + Mechanical energy

$$Lidi + i^2dL = Lidi + \frac{1}{2}i^2dL + T_d d\theta \tag{1.27}$$

$$\frac{1}{2}i^2dL = T_d d\theta \tag{1.28}$$

$$T = \frac{1}{2}i^2 \frac{dL}{d\theta} \tag{1.29}$$

At steady state condition $T_d = T_C$

$$\frac{1}{2}i^2 \frac{dL}{d\theta} = K\theta \tag{1.30}$$

$$\theta = \frac{1}{2K}i^2 \frac{dL}{d\theta} \tag{1.31}$$

$$\theta \propto i^2 \tag{1.32}$$

When the instruments measure AC, $\theta \propto i_{rms}^2$

Scale of the instrument is non uniform.

Advantages

- ✓ MI can be used in AC and DC
- ✓ It is cheap
- ✓ Supply is given to a fixed coil, not in moving coil.
- ✓ Simple construction
- ✓ Less friction error.

Disadvantages

- ✓ It suffers from eddy current and hysteresis error
- ✓ Scale is not uniform
- ✓ It consumed more power
- ✓ Calibration is different for AC and DC operation


Repulsion type moving iron instrument

Construction: The repulsion type instrument has a hollow fixed iron attached to it (Fig. 1.12). The moving iron is connected to the spindle. The pointer is also attached to the spindle in supported with jeweled bearing.

Principle of operation: When the current flows through the coil, a magnetic field is produced by it. So both fixed iron and moving iron are magnetized with the same polarity, since they are kept in the same magnetic field. Similar poles of fixed and moving iron get repelled. Thus the deflecting torque is produced due to magnetic repulsion. Since moving iron is attached to spindle, the spindle will move. So that pointer moves over the calibrated scale.

Damping: Air friction damping is used to reduce the oscillation.

Control: Spring control is used.

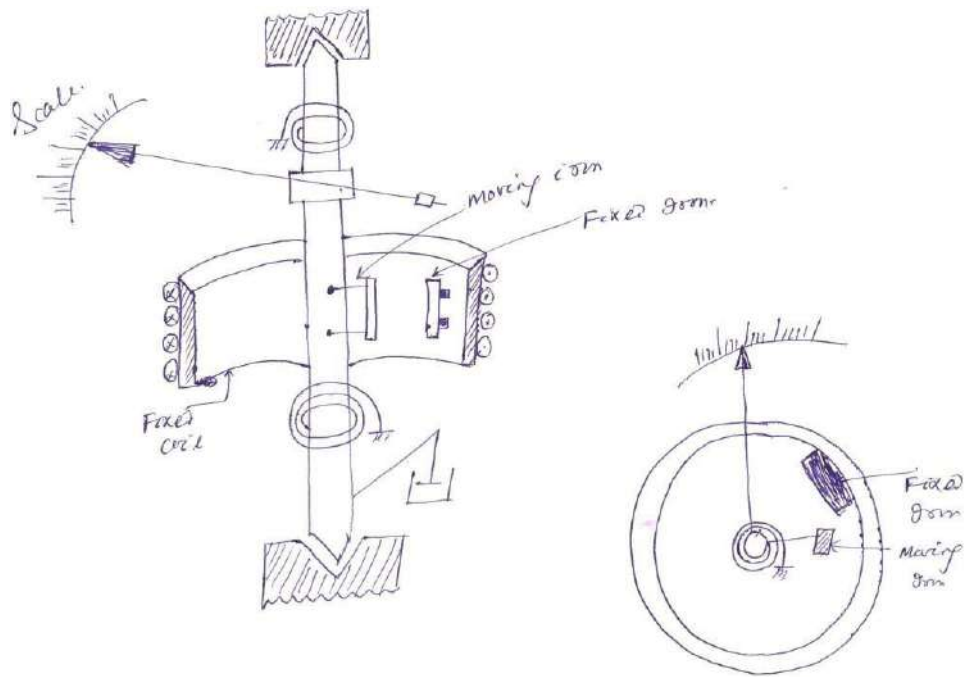

Errors in PMMC

- ✓ The permanent magnet produced error due to ageing effect. By heat treatment, this error can be eliminated.
- ✓ The spring produces error due to ageing effect. By heat treating the spring the error can be eliminated.
- ✓ When the temperature changes, the resistance of the coil vary and the spring also produces error in deflection. This error can be minimized by using a spring whose temperature co-efficient is very low.

Difference between attraction and repulsion type instrument

An attraction type instrument will usually have a lower inductance, compare to repulsion type instrument. But in other hand, repulsion type instruments are more suitable for economical production in manufacture and nearly uniform scale is more easily obtained. They are therefore much more common than attraction type.

Error in M.I instrument

Temperature error

Due to temperature variation, the resistance of the coil varies. This affects the deflection of the instrument. The coil should be made of manganin, so that the resistance is almost constant.

Hysteresis error

Due to hysteresis affect the reading of the instrument will not be correct. When the current is decreasing, the flux produced will not decrease suddenly. Due to this the meter reads a higher value of current. Similarly when the current increases the meter reads a lower value of current. This produces error in deflection. This error can be eliminated using small iron parts with narrow hysteresis loop so that the demagnetization takes place very quickly.

Eddy current error

The eddy currents induced in the moving iron affect the deflection. This error can be reduced by increasing the resistance of the iron.

Stray field error


Since the operating field is weak, the effect of stray field is more. Due to this, error is produced in deflection. This can be eliminated by shielding the parts of the instrument.

Basic principle of operation of DC Ammeter:

Current is the rate of flow of electric charge. If this electric charge flows only in one direction, then the resultant current is called Direct Current (DC). The instrument, which is used to measure the Direct Current called **DC ammeter**.

If we place a resistor in parallel with the Permanent Magnet Moving Coil (PMMC) galvanometer, then the entire combination acts as DC ammeter. The parallel resistance, which is used in DC ammeter is also called shunt resistance or simply, **shunt**. The value of this resistance should be considered small in order to measure the DC current of large value.

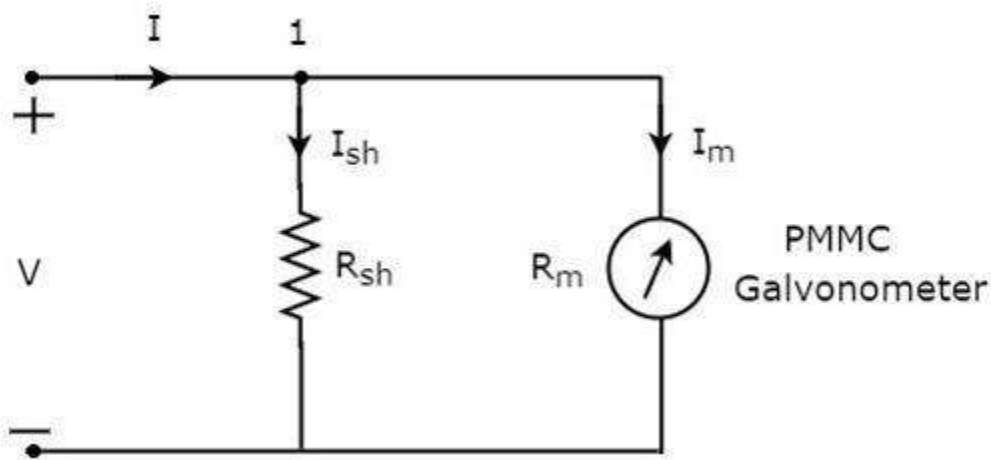The **circuit diagram** of DC ammeter is shown in below figure.



We have to place this **DC ammeter** in series with the branch of an electric circuit, where the DC current is to be measured.

the voltage across the elements, which are connected in parallel is same. So, the voltage across shunt resistor, R_{sh} and the voltage across galvanometer resistance, R_m is same, since those two elements are connected in parallel in above circuit.

Mathematically, it can be written as $I_{sh}R_{sh}=I_mR_m$

$$\Rightarrow R_{sh} = \frac{I_m R_m}{I_{sh}} \quad \text{Equation 1}$$

The **KCL equation** at node 1 is

$$-I + I_{sh} + I_m = 0$$

$$\Rightarrow I_{sh} = I - I_m$$

Substitute the value of I_{sh} in Equation 1.

$$R_{sh} = \frac{I_m R_m}{I - I_m} \quad \text{Equation 2}$$

Take, I_m as common in the denominator term, which is present in the right hand side of Equation 2.

$$R_{sh} = \frac{I_m R_m}{I_m \left(\frac{I}{I_m} - 1 \right)}$$

$$\Rightarrow R_{sh} = \frac{R_m}{\frac{I}{I_m} - 1} \quad \text{Equation 3}$$

Where,

R_{sh} is the shunt resistance

R_m is the internal resistance of galvanometer

I is the total Direct Current that is to be measured

I_m is the full scale deflection current

The ratio of total Direct Current that is to be measured, I and the full scale deflection current of the galvanometer, I_m is known as **multiplying factor, m**. Mathematically, it can be represented as

$$m = \frac{I}{I_m} \quad \text{Equation 4}$$

Equation 3 looks like as below after substituting Equation 4 in Equation 3.


$$R_{sh} = \frac{R_m}{m - 1} \quad \text{Equation 5}$$

We can find the **value of shunt resistance** by using either Equation 2 or Equation 5 based on the available data.

Multi Range DC Ammeter:

In previous section, we discussed about DC ammeter which is obtained by placing a resistor in parallel with the PMMC galvanometer. This DC ammeter can be used to measure a **particular range** of Direct Currents.

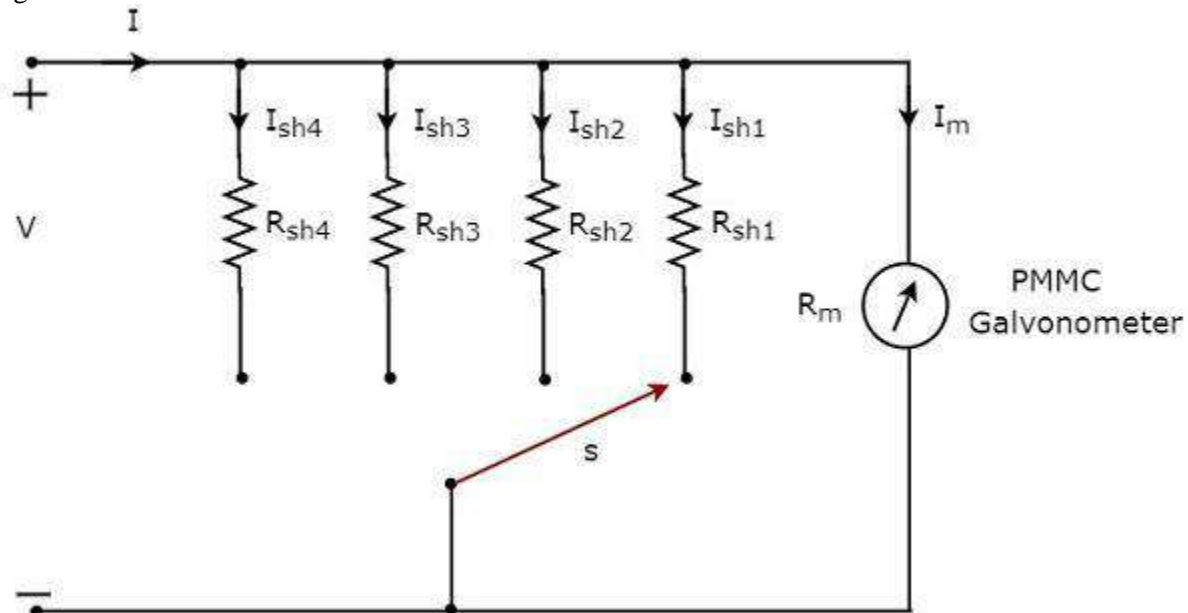If we want to use the DC ammeter for measuring the Direct Currents of **multiple ranges**, then we have to use multiple parallel resistors instead of single resistor and this entire combination of resistors is in parallel to the PMMC galvanometer. The **circuit diagram** of multi range DC ammeter is shown in below figure.



Place this multi range DC ammeter in series with the branch of an electric circuit, where the Direct Current of required range is to be measured. The desired range of currents is chosen by connecting the switch, *s* to the respective shunt resistor.

Let, m_1 , m_2 , m_3 and m_4 are the **multiplying factors** of DC ammeter when we consider the total Direct Currents to be measured as I_1 , I_2 , I_3 and I_4 respectively. Following are the formulae corresponding to each multiplying factor.

$$m_1 = \frac{I_1}{I_m}$$

$$m_2 = \frac{I_2}{I_m}$$

$$m_3 = \frac{I_3}{I_m}$$

$$m_4 = \frac{I_4}{I_m}$$

In above circuit, there are four **shunt resistors**, R_{sh1} , R_{sh2} , R_{sh3} and R_{sh4} . Following are the formulae corresponding to these four resistors.

$$R_{sh1} = \frac{R_m}{m_1 - 1}$$

$$R_{sh2} = \frac{R_m}{m_2 - 1}$$

$$R_{sh3} = \frac{R_m}{m_3 - 1}$$

$$R_{sh4} = \frac{R_m}{m_4 - 1}$$

The above formulae will help us find the resistance values of each shunt resistor.

Basic principle of operation of AC Ammeter:

Current is the rate of flow of electric charge. If the direction of this electric charge changes regularly, then the resultant current is called **Alternating Current (AC)**.


The instrument, which is used to measure the Alternating Current that flows through any branch of electric circuit is called **AC ammeter**.

Example: Thermocouple type AC ammeter


Now, let us discuss about Thermocouple type AC ammeter.

Thermocouple Type AC Ammeter:

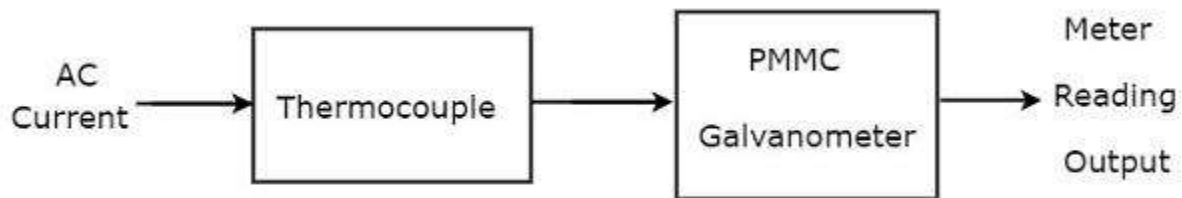If a Thermocouple is connected ahead of PMMC galvanometer, then that entire combination is called thermocouple type AC ammeter. The **block diagram** of thermocouple type AC ammeter is shown in below figure.



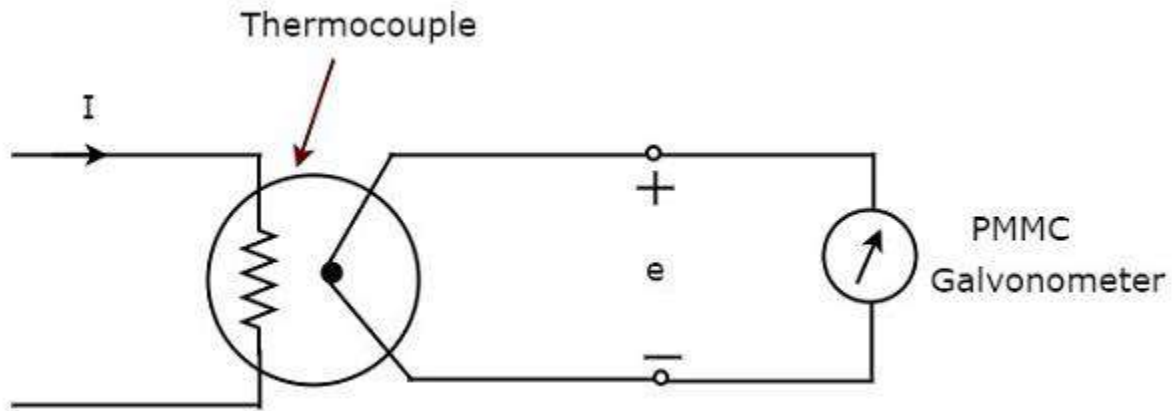The above block diagram consists of mainly two blocks: a thermocouple, and a PMMC galvanometer. We will get the corresponding circuit diagram, just by replacing each block with the respective component(s) in above block diagram. So, the **circuit diagram** of thermocouple type AC ammeter will look like as shown in below figure.




Thermocouple generates an EMF, e , whenever the Alternating Current, I flows through heater element. This EMF, e is directly proportional to the rms value of the current, I that is flowing through heater element. So, we have to calibrate the scale of PMMC instrument to read **rms values of current**. So, with this chapter we have completed all basic measuring instruments such as DC voltmeters, AC voltmeters, DC ammeters and AC ammeters. In next chapter, let us discuss about the meters or measuring instruments, which measure resistance value

Basic principle of operation of DC Voltmeter:

DC voltmeter is a measuring instrument, which is used to measure the DC voltage across any two points of electric circuit. If we place a resistor in series with the Permanent Magnet Moving Coil (PMMC) galvanometer, then the entire combination together acts as **DC voltmeter**.

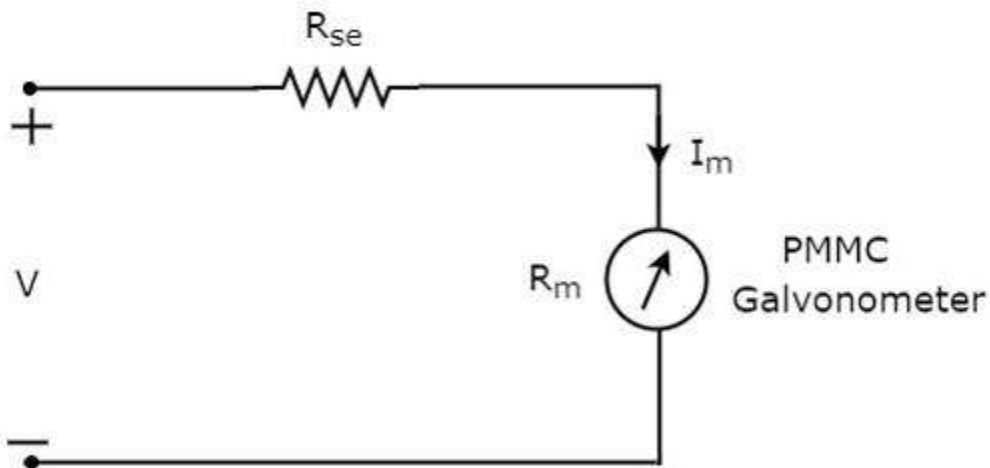The series resistance, which is used in DC voltmeter is also called series multiplier resistance or simply, multiplier. It basically limits the amount of current that flows through galvanometer in order to prevent the meter current from exceeding the full scale deflection value. The **circuit diagram** of DC voltmeter is shown in below figure.



We have to place this DC voltmeter across the two points of an electric circuit, where the DC voltage is to be measured. Apply **KVL** around the loop of above circuit.

$$V - I_m R_{se} - I_m R_m = 0 \quad \text{Equation 1}$$

$$\Rightarrow V - I_m R_m = I_m R_{se}$$

$$\Rightarrow R_{se} = \frac{V - I_m R_m}{I_m}$$

$$\Rightarrow R_{se} = \frac{V}{I_m} - R_m \quad \text{Equation 2}$$

Where,

R_{se} is the series multiplier resistance

V is the full range DC voltage that is to be measured

I_m is the full scale deflection current

R_m is the internal resistance of galvanometer

The ratio of full range DC voltage that is to be measured, V and the DC voltage drop across the galvanometer, V_m is known as **multiplying factor, m**.

Mathematically, it can be represented as

$$m = \frac{V}{V_m} \quad \text{Equation 3}$$

From Equation 1, we will get the following equation for **full range DC voltage** that is to be measured, **V**.

$$V = I_m R_{se} + I_m R_m \quad \text{Equation 4}$$

The **DC voltage drop** across the galvanometer, V_m is the product of full scale deflection current, I_m and internal resistance of galvanometer, R_m . Mathematically, it can be written as

$$V_m = I_m R_m \quad \text{Equation 5}$$

Substitute, Equation 4 and Equation 5 in Equation 3.

$$m = \frac{I_m R_{se} + I_m R_m}{I_m R_m}$$

$$\Rightarrow m = \frac{R_{se}}{R_m} + 1$$

$$\Rightarrow m - 1 = \frac{R_{se}}{R_m}$$


$$\Rightarrow R_{se} = R_m (m - 1) \quad \text{Equation 6}$$

We can find the **value of series multiplier resistance** by using either Equation 2 or Equation 6 based on the available data.

Multi Range DC Voltmeter:

In previous section, we had discussed DC voltmeter, which is obtained by placing a multiplier resistor in series with the PMMC galvanometer. This DC voltmeter can be used to measure a **particular range** of DC voltages.

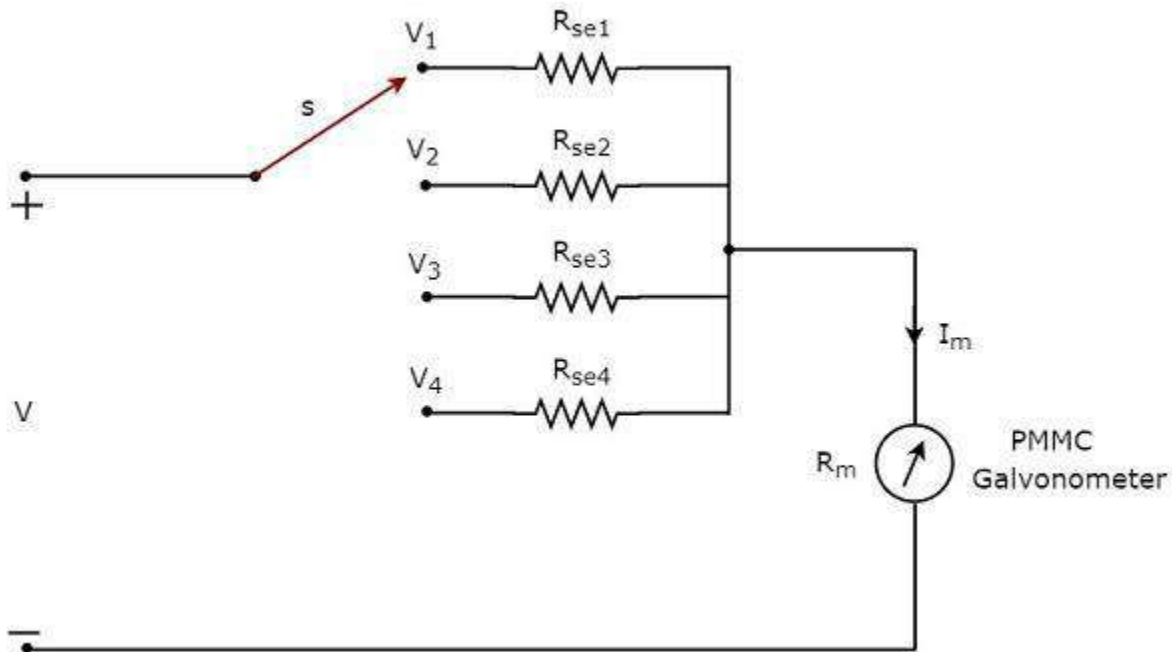If we want to use the DC voltmeter for measuring the DC voltages of **multiple ranges**, then we have to use multiple parallel multiplier resistors instead of single multiplier resistor and this entire combination of resistors is in series with the PMMC galvanometer. The **circuit diagram** of multi range DC voltmeter is shown in below figure



We have to place this **multi range DC voltmeter** across the two points of an electric circuit, where the DC voltage of required range is to be measured. We can choose the desired range of voltages by connecting the switch s to the respective multiplier resistor.

Let, m_1 , m_2 , m_3 and m_4 are the **multiplying factors** of DC voltmeter when we consider the full range DC voltages to be measured as, V_1 , V_2 , V_3 and V_4 respectively. Following are the formulae corresponding to each multiplying factor.

$$m_1 = \frac{V_1}{V_m}$$

$$m_2 = \frac{V_2}{V_m}$$

$$m_3 = \frac{V_3}{V_m}$$

$$m_4 = \frac{V_4}{V_m}$$

In above circuit, there are four **series multiplier resistors**, R_{se1} , R_{se2} , R_{se3} and R_{se4} . Following are the formulae corresponding to these four resistors.

$$R_{se1} = R_m(m_1 - 1)$$

$$R_{se2} = R_m(m_2 - 1)$$

$$R_{se3} = R_m(m_3 - 1)$$

$$R_{se4} = R_m(m_4 - 1)$$

So, we can find the resistance values of each series multiplier resistor by using above formulae.

Basic principle of operation of AC Voltmeter :

The instrument, which is used to measure the AC voltage across any two points of electric circuit is called **AC voltmeter**. If the AC voltmeter consists of rectifier, then it is said to be rectifier based AC voltmeter. The DC voltmeter measures only DC voltages. If we want to use it for measuring AC voltages, then we have to follow these two steps.

• **Step1:** Convert the AC voltage signal into a DC voltage signal by using a rectifier.

▣ **Step2:** Measure the DC or average value of the rectifier's output signal.

We get **Rectifier based AC voltmeter**, just by including the rectifier circuit to the basic DC voltmeter. This chapter deals about rectifier based AC voltmeters.

Types of Rectifier based AC Voltmeters:


Following are the **two types** of rectifier based AC voltmeters.

- AC voltmeter using Half Wave Rectifier
- AC voltmeter using Full Wave Rectifier


Now, let us discuss about these two AC voltmeters one by one.

AC Voltmeter using Half Wave Rectifier:

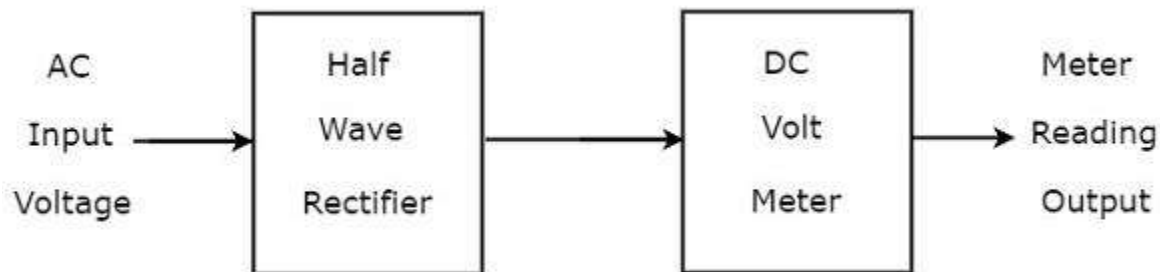If a Half wave rectifier is connected ahead of DC voltmeter, then that entire combination together is called AC voltmeter using Half wave rectifier. The **block diagram** of AC voltmeter using Half wave rectifier is shown in below figure.



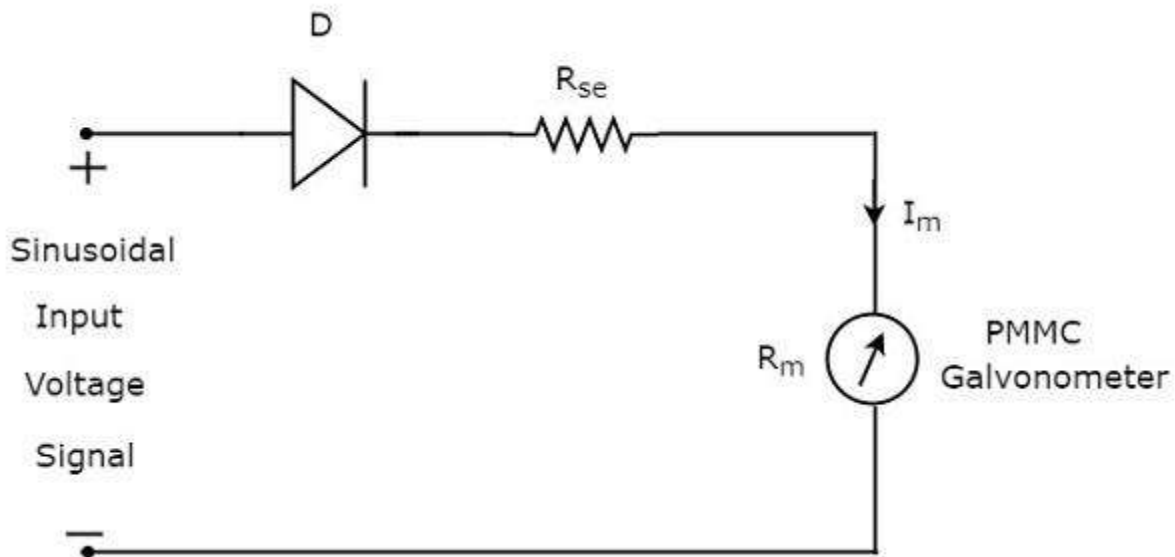The above block diagram consists of two blocks: half wave rectifier and DC voltmeter. We will get the corresponding circuit diagram, just by replacing each block with the respective component(s) in above block diagram. So, the **circuit diagram** of AC voltmeter using Half wave rectifier will look like as shown in below figure.



The **rms value** of sinusoidal (AC) input voltage signal is

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$\Rightarrow V_m = \sqrt{2} V_{rms}$$

$$\Rightarrow V_m = 1.414 V_{rms}$$

Where,

V_m is the maximum value of sinusoidal (AC) input voltage signal.

The **DC** or average value of the Half wave rectifier's output signal is

$$V_{dc} = \frac{V_m}{\pi}$$

Substitute, the value of V_m in above equation.


$$V_{dc} = 1.414 V_{rms} / \pi$$

$$V_{dc} = 0.45 V_{rms}$$

Therefore, the AC voltmeter produces an output voltage, which is equal to **0.45** times the rms value of the sinusoidal (AC) input voltage signal.


AC Voltmeter using Full Wave Rectifier:

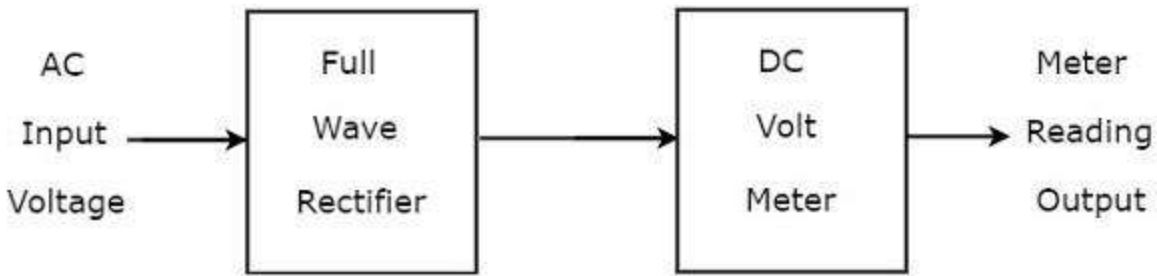If a Full wave rectifier is connected ahead of DC voltmeter, then that entire combination together is called AC voltmeter using Full wave rectifier. The **block diagram** of AC voltmeter using Full wave rectifier is shown in below figure.



The above block diagram consists of two blocks: full wave rectifier and DC voltmeter. We will get the corresponding circuit diagram just by replacing each block with the respective component(s) in above block diagram.

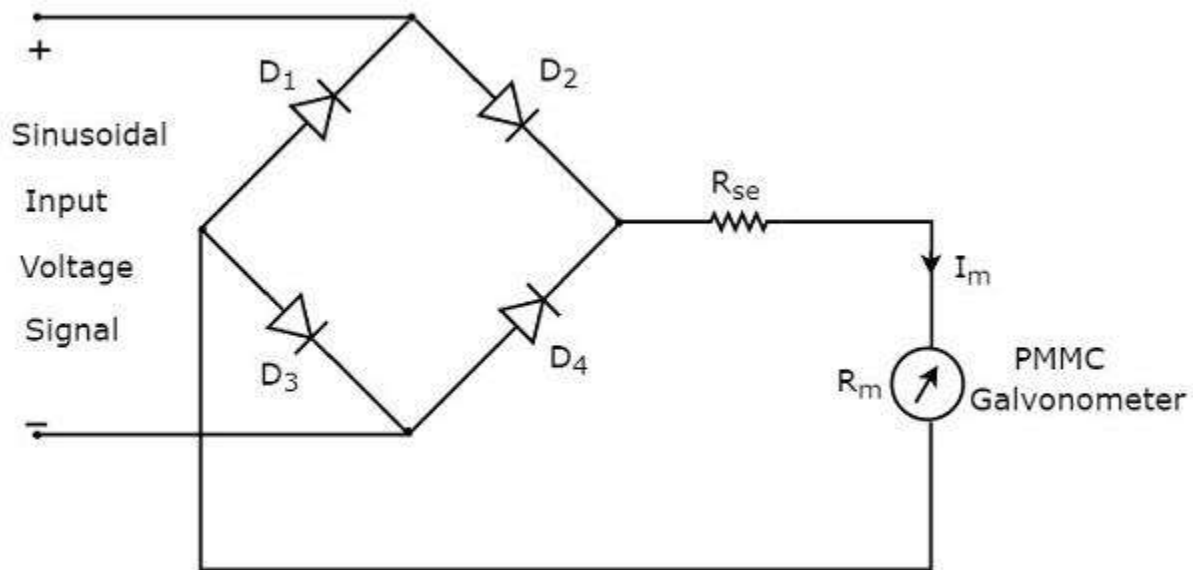So, the **circuit diagram** of AC voltmeter using Full wave rectifier will look like as shown in below figure.



The **rms value** of sinusoidal (AC) input voltage signal is

$$V_{rms} = V_m / \sqrt{2}$$

$$\Rightarrow V_m = \sqrt{2} V_{rms}$$

$$\Rightarrow V_m = 1.414 V_{rms}$$

Where,

V_m is the maximum value of sinusoidal (AC) input voltage signal.

The **DC** or average value of the Full wave rectifier's output signal is

$$V_{dc} = \frac{2V_m}{\pi}$$

Substitute, the value of V_m in above equation.

$$V_{dc} = \frac{2 \times 1.414 V_{rms}}{\pi}$$

$$V_{dc} = 0.9 V_{rms}$$

Therefore, the AC voltmeter produces an output voltage, which is equal to **0.9** times the rms value of the sinusoidal (AC) input voltage signal.

Basic principle of Ohm Meter:

The instrument, which is used to measure the value of resistance between any two points in an electric circuit is called **ohmmeter**. It can also be used to find the value of an unknown resistor. The units of resistance are ohm and the measuring instrument is meter. So, the word “ohmmeter” is obtained by combining the words “ohm” and “meter”.

Types of Ohmmeters:


Following are the **two types** of ohmmeters.

- Series Ohmmeter
- Shunt Ohmmeter

Now, let us discuss about these two types of ohmmeters one by one.

Series Ohmmeter:

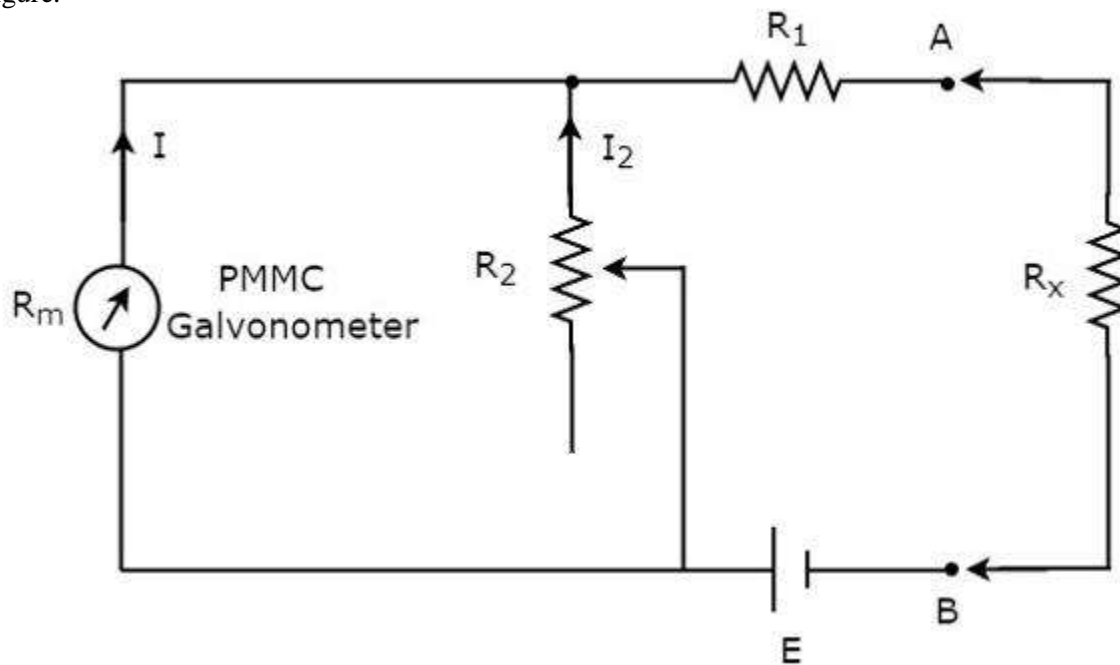If the resistor's value is unknown and has to be measured by placing it in series with the ohmmeter, then that ohmmeter is called series ohmmeter. The **circuit diagram** of series ohmmeter is shown in below figure.



The part of the circuit, which is left side of the terminals A & B is **series ohmmeter**. So, we can measure the value of unknown resistance by placing it to the right side of terminals A & B . Now, let us discuss about the **calibration scale** of series ohmmeter.


- If $R_x = 0 \Omega$, then the terminals A & B will be short circuited with each other. So, the meter current gets divided between the resistors, R_1 and R_2 . Now, vary the value of resistor, R_2 in such a way that the entire meter current flows through the resistor, R_1 only. In this case, the meter shows **full scale deflection current**. Hence, this full scale deflection current of the meter can be represented as **0Ω** .

- If $R_x = \infty \Omega$, then the terminals A & B will be open circuited with each other. So, no current flows through resistor, R_1 . In this case, the meter shows **null deflection current**. Hence, this null deflection of the meter can be represented as **$\infty \Omega$** .

- In this way, by considering different values of R_x , the meter shows different deflections. So, accordingly we can represent those deflections with the corresponding resistance value. The series ohmmeter consists of a calibration scale. It has the indications of 0Ω and $\infty \Omega$ at the end points of right hand and left hand of the scale respectively. Series ohmmeter is useful for measuring **high values of resistances**.

Shunt Ohmmeter:

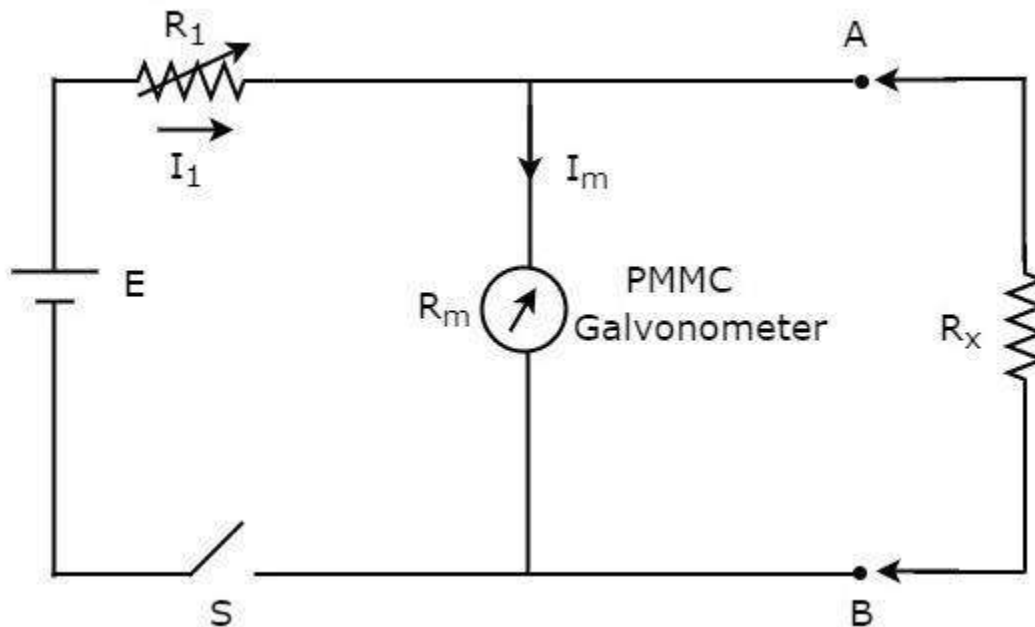If the resistor's value is unknown and to be measured by placing it in parallel (shunt) with the ohmmeter, then that ohmmeter is called shunt ohmmeter. The **circuit diagram** of shunt ohmmeter is shown in below figure.



The part of the circuit, which is left side of the terminals A & B is **shunt ohmmeter**. So, we can measure the value of unknown resistance by placing it to the right side of terminals A & B.

Now, let us discuss about the **calibration scale** of shunt ohmmeter. Close the switch, S of above circuit while it is in use.

- If $R_x=0 \Omega$, then the terminals A & B will be short circuited with each other. Due to this, the entire current, I_1 flows through the terminals A & B. In this case, no current flows through PPMC galvanometer. Hence, the **null deflection** of the PPMC galvanometer can be represented as **0Ω** .
- If $R_x=\infty \Omega$, then the terminals A & B will be open circuited with each other. So, no current flows through the terminals A & B. In this case, the entire current, I_1 flows through PPMC galvanometer. If required vary (adjust) the value of resistor, R_1 until the PPMC galvanometer shows full scale deflection current. Hence, this **full scale deflection** current of the PPMC galvanometer can be represented as **$\infty \Omega$** .
- In this way, by considering different values of R_x , the meter shows different deflections. So, accordingly we can represent those deflections with the corresponding resistance values. The shunt ohmmeter consists of a calibration scale. It has the indications of 0Ω and $\infty \Omega$ at the end points of left hand and right hand of the scale respectively. Shunt ohmmeter is useful for measuring **low values of resistances**. So, we can use either series ohmmeter or shunt ohmmeter based on the values of resistances that are to be measured i.e., high or low.

Basic principle of Analog Multimeter, its types & applications:

In previous chapters, we discussed about voltmeters, ammeters and ohmmeters. These measuring instruments are used to measure voltage, current and resistance respectively. That means, we have **separate measuring instruments** for measuring voltage, current and resistance.


Suppose, if a single measuring instrument can be used to measure the quantities such as voltage, current & resistance one at a time, then it is said to be **multimeter**. It has got the name multimeter, since it can measure multiple electrical quantities one at a time.

Measurements by using Multimeter:

Multimeter is an instrument used to measure DC & AC voltages, DC & AC currents and resistances of several ranges. It is also called Electronic Multimeter or Voltage Ohm Meter (VOM).

DC voltage Measurement:

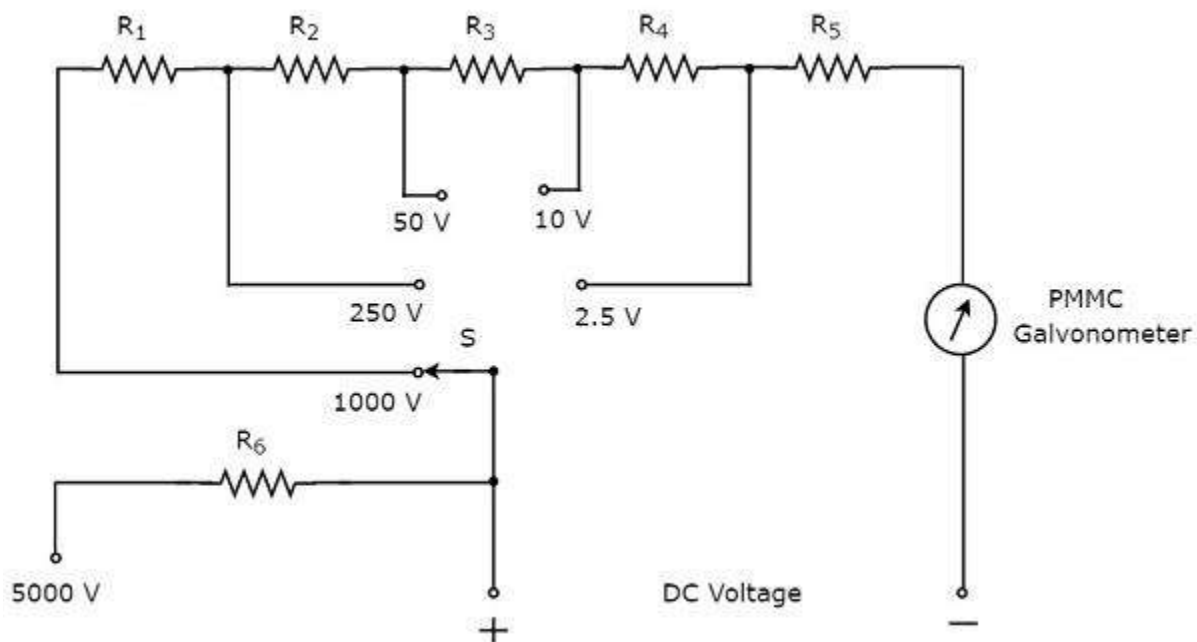The part of the **circuit diagram** of Multimeter, which can be used to measure DC voltage is shown in below figure.




The above circuit looks like a multi range DC voltmeter. The combination of a resistor in series with PMMC galvanometer is a **DC voltmeter**. So, it can be used to measure DC voltages up to certain value. We can increase the range of DC voltages that can be measured with the same DC voltmeter by increasing the resistance value. the equivalent resistance value increases, when we connect the resistors are in **series**.

In above circuit, we can measure the DC voltages up to **2.5V** by using the combination of resistor, R_5 in series with PMMC galvanometer. By connecting a resistor, R_4 in series with the previous circuit, we can measure the DC voltages up to **10V**. In this way, we can increase the range of DC voltages, simply by connecting a resistor in series with the previous (earlier) circuit.

We can measure the DC voltage across any two points of an electric circuit, by connecting the switch, S to the desired voltage range.

DC Current Measurement:

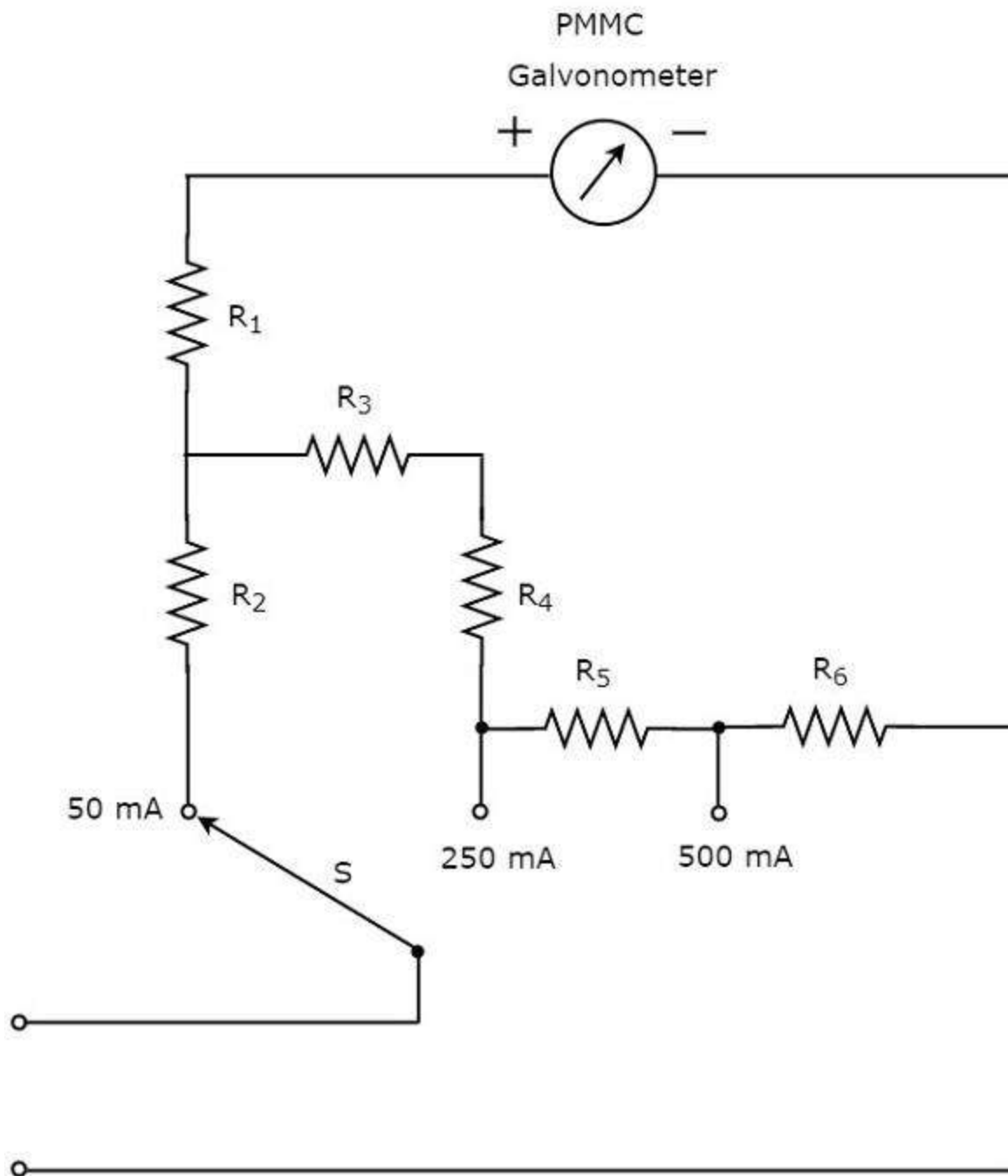
The part of the **circuit diagram** of Multimeter, which can be used to measure DC current is shown in below figure.



The above circuit looks like a multi range DC ammeter. the combination of a resistor in parallel with PMMC galvanometer is a **DC ammeter**. So, it can be used to measure DC currents up to certain value. We can get **different ranges** of DC currents measured with the same DC ammeter by placing the resistors in parallel with previous resistor. In above circuit, the resistor, R_1 is connected in series with the PMMC galvanometer in order to prevent the meter gets damaged due to large current. We can measure the DC current that is flowing through any two points of an electric circuit, by connecting the switch, S to the desired current range.

AC voltage Measurement:

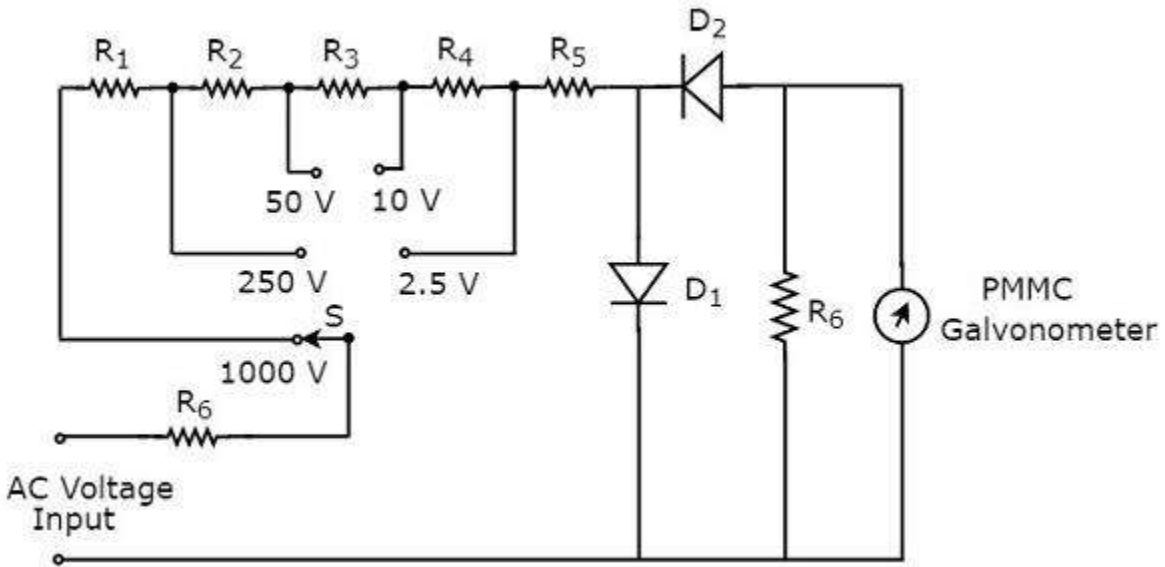The part of the **circuit diagram** of Multimeter, which can be used to measure AC voltage is shown in below figure.




The above circuit looks like a **multi range AC voltmeter**. We know that, we will get AC voltmeter just by placing rectifier in series (cascade) with DC voltmeter. The above circuit was created just by placing the diodes combination and resistor, R_6 in between resistor, R_5 and PMMC galvanometer.

We can measure the AC voltage across any two points of an electric circuit, by connecting the switch, S to the desired voltage range.

Resistance Measurement:

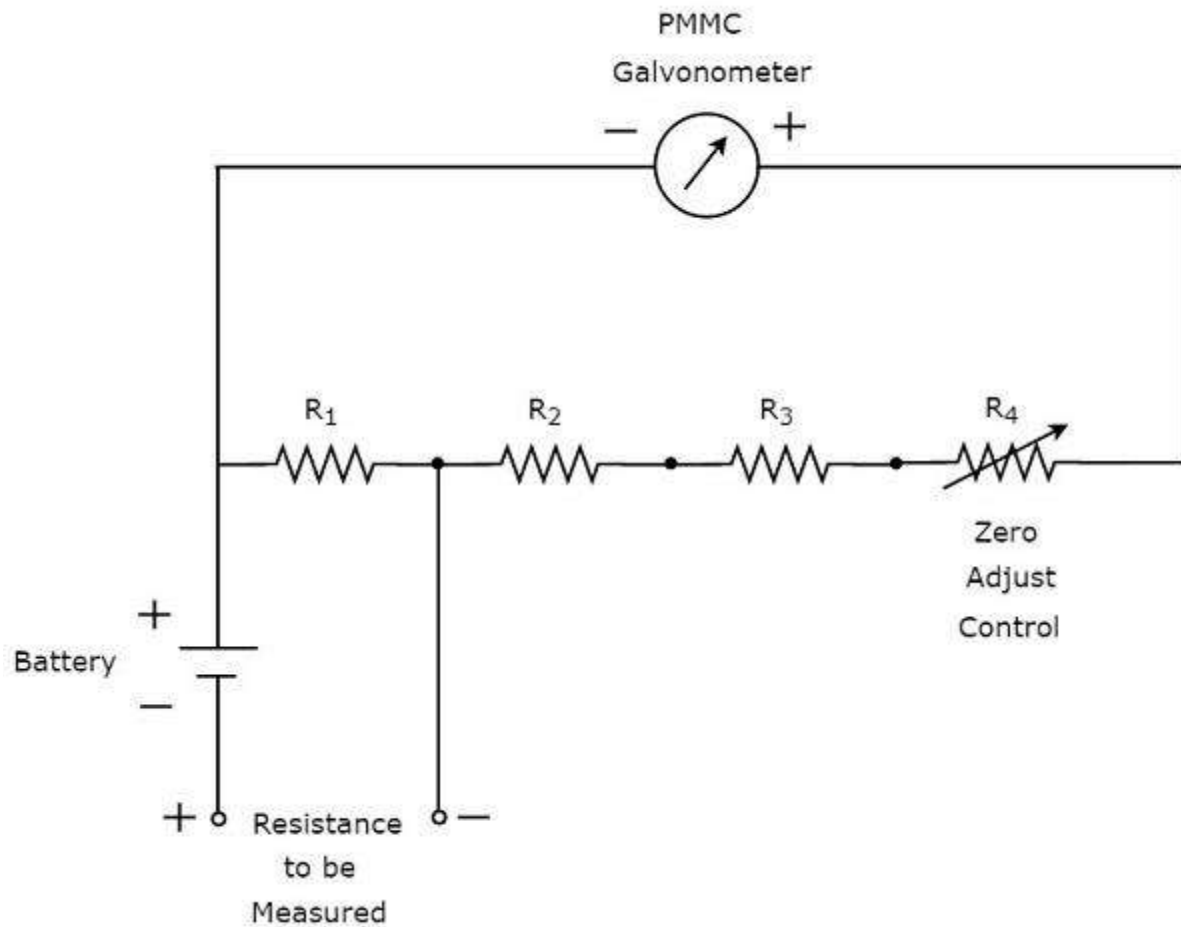The part of the **circuit diagram** of Multimeter, which can be used to measure resistance is shown in below figure.



We have to do the following two tasks before taking any measurement

☐ Short circuit the instrument

- Vary the zero adjust control until the meter shows full scale current. That means, meter indicates zero resistance value.


Now, the above circuit behaves as shunt ohmmeter and has the scale multiplication of 1, i.e. 100. We can also consider higher order powers of 10 as the scale multiplications for measuring high resistances.

UNIT-4
OSCILLOSCOPE

Oscilloscope is an electronic equipment, which displays a voltage waveform. Among the oscilloscopes, Cathode Ray Oscilloscope (CRO) is the basic one and it displays a time varying signal or waveform.

Block Diagram of CRO

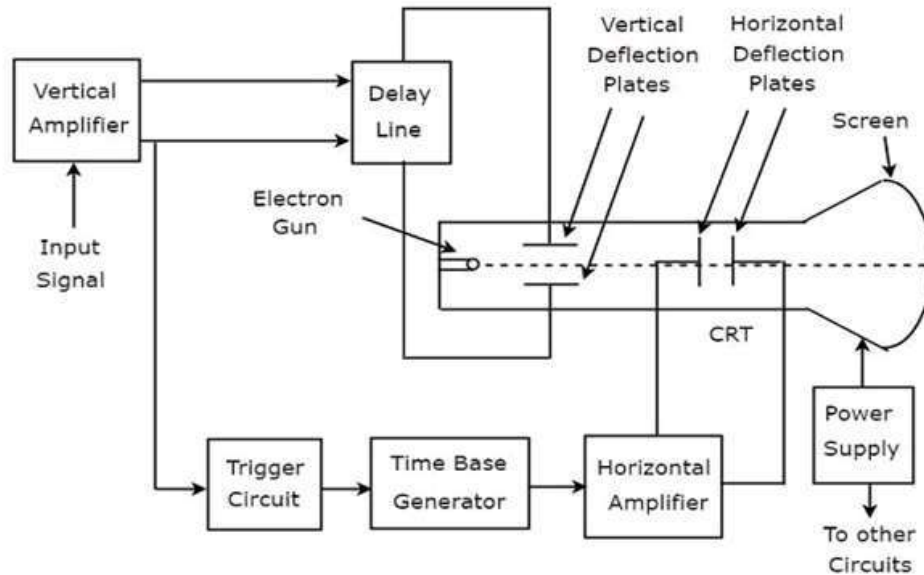Cathode Ray Oscilloscope (CRO) consists a set of blocks. Those are vertical amplifier, delay line, trigger circuit, time base generator, horizontal amplifier, Cathode Ray Tube (CRT) & powersupply. The **block diagram** of CRO is shown in below figure



The **function** of each block of CRO is mentioned below.

- **Vertical Amplifier:** It amplifies the input signal, which is to be displayed on the screen of CRT.

- ☐ **Delay Line:** It provides some amount of delay to the signal, which is obtained at the output of vertical amplifier. This delayed signal is then applied to vertical deflection plates of CRT.

- ☐ **Trigger Circuit:** It produces a triggering signal in order to synchronize both horizontal and vertical deflections of electron beam.

- **Time base Generator:** It produces a saw tooth signal, which is useful for horizontal deflection of electron beam.

- ☐ **Horizontal Amplifier:** It amplifies the saw tooth signal and then connects it to the horizontal deflection plates of CRT.

- ☐ **Power supply:** It produces both high and low voltages. The negative high voltage and positive low voltage are applied to CRT and other circuits respectively.

- **Cathode Ray Tube (CRT):** It is the major important block of CRO and mainly consists of four parts. Those are electron gun, vertical deflection plates, horizontal deflection plates and fluorescent screen.

The electron beam, which is produced by an electron gun gets deflected in both vertical and horizontal directions by a pair of vertical deflection plates and a pair of horizontal deflection plates respectively. Finally, the deflected beam will appear as a spot on the fluorescent screen.

In this way, CRO will display the applied input signal on the screen of CRT. So, we can analyse the signals in time domain by using CRO.

Measurements by using CRO:

We can do the following measurements by using CRO.

Measurement of Amplitude

Measurement of Time Period

Measurement of Frequency

Measurement of Amplitude

CRO displays the voltage signal as a function of time on its screen. The **amplitude** of that voltage signal is constant, but we can vary the number of divisions that cover the voltage signal in vertical direction by varying **volt/division** knob on the CRO panel. Therefore, we will get the **amplitude** of the signal, which is present on the screen of CRO by using following formula.

$$A=j \times n_v$$

Where,

A is the amplitude

j is the value of volt/division

n_v is the number of divisions that cover the signal in vertical direction.

Measurement of Time Period

CRO displays the voltage signal as a function of time on its screen. The **Time period** of that periodic voltage signal is constant, but we can vary the number of divisions that cover one complete cycle of voltage signal in horizontal direction by varying **time/division** knob on the CRO panel.

Therefore, we will get the **Time period** of the signal, which is present on the screen of CRO by using following formula.

$$T=k \times n_h$$

Where,

T is the Time period

k is the value of time/division

n_h is the number of divisions that cover one complete cycle of the periodic signal in horizontal direction.

Measurement of Frequency

The frequency, f of a periodic signal is the reciprocal of time period, T .

Mathematically, it can be represented as $f=1/T$

So, we can find the frequency, f of a periodic signal by following these two steps.

Step1: Find the **Time period** of periodic signal.


Step2: Take **reciprocal** of Time period of periodic signal, which is obtained in Step1.

Lissajous figures:

Lissajous figure is the pattern which is displayed on the screen, when sinusoidal signals are applied to both horizontal & vertical deflection plates of CRO. These patterns will vary based on the amplitudes, frequencies and phase differences of

the sinusoidal signals, which are applied to both horizontal & vertical deflection plates of CRO.

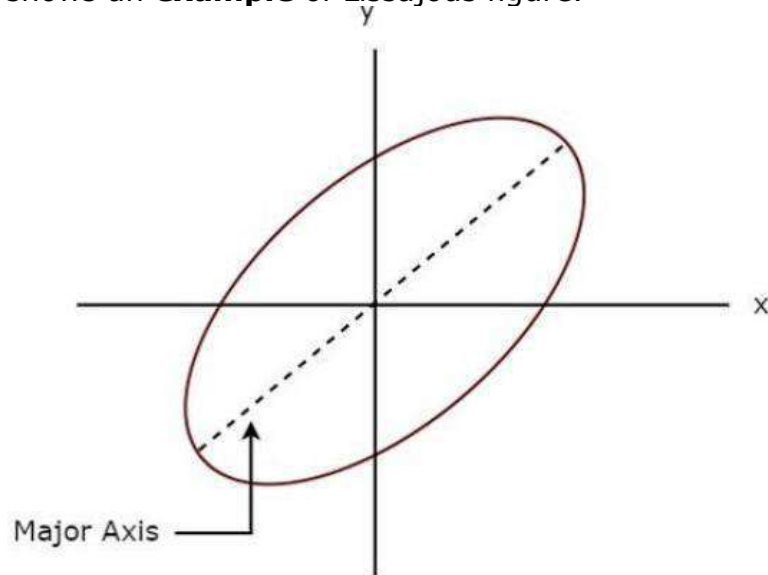The following figure shows an **example** of Lissajous figure.



The above Lissajous figure is in **elliptical shape** and its major axis has some inclination angle with positive x-axis.

Measurements using Lissajous Figures:

We can do the following **two measurements** from a Lissajous figure.

- Frequency of the sinusoidal signal
- Phase difference between two sinusoidal signals

Now, let us discuss about these two measurements one by one.

Measurement of Frequency

Lissajous figure will be displayed on the screen, when the sinusoidal signals are applied to both horizontal & vertical deflection plates of CRO. Hence, apply the sinusoidal signal, which has standard **known frequency** to the horizontal deflection plates of CRO. Similarly, apply the sinusoidal signal, whose **frequency is unknown** to the vertical deflection plates of CRO.

Let, f_H and f_V are the frequencies of sinusoidal signals, which are applied to the horizontal & vertical deflection plates of CRO respectively. The relationship between f_H and f_V can be **mathematically** represented as below.

$$f_V/f_H = n_H/n_V$$

From above relation, we will get the frequency of sinusoidal signal, which is applied to the vertical deflection plates of CRO as

Where,

n_H is the number of horizontal tangencies

n_V is the number of vertical tangencies

We can find the values of n_H and n_V from Lissajous figure. So, by substituting the values of n_H , n_V and f_H in Equation 1, we will get the value of f_V , i.e. the **frequency of sinusoidal signal** that is applied to the vertical deflection plates of CRO.

Measurement of Phase Difference:

A Lissajous figure is displayed on the screen when sinusoidal signals are applied to both horizontal & vertical deflection plates of CRO. Hence, apply the sinusoidal signals, which have **same amplitude and frequency** to both horizontal and vertical deflection plates of CRO.

For few Lissajous figures based on their shape, we can directly tell the phase difference between the two sinusoidal signals.

□ If the Lissajous figure is a **straight line** with an inclination of **45°** with positive x-axis, then the **phase difference** between the two sinusoidal signals will be **0°**. That means, there is no phase difference between those two sinusoidal signals.

If the Lissajous figure is a **straight line** with an inclination of **135°** with positive x-axis, then the **phase difference** between the two sinusoidal signals will be **180°**. That means, those two sinusoidal signals are out of phase.

▣ If the Lissajous figure is in **circular shape**, then the phase difference between the two sinusoidal signals will be **90°** or **270°**.

We can calculate the phase difference between the two sinusoidal signals by using formulae, when the Lissajous figures are of **elliptical shape**.

If the major axis of an elliptical shape Lissajous figure having an inclination angle lies between **0°** and **90°** with positive x-axis, then the phase difference between the two sinusoidal signals will be

$$\phi = \sin^{-1} \left(\frac{x_1}{x_2} \right) = \sin^{-1} \left(\frac{y_1}{y_2} \right)$$

If the major axis of an elliptical shape Lissajous figure having an inclination angle lies between **90°** and **180°** with positive x-axis, then the phase difference between the two sinusoidal signals will be

$$\phi = 180^\circ - \sin^{-1} \left(\frac{x_1}{x_2} \right) = 180^\circ - \sin^{-1} \left(\frac{y_1}{y_2} \right)$$

Where,

x_1 is the distance from the origin to the point on x-axis, where the elliptical shape Lissajous figure intersects

x_2 is the distance from the origin to the vertical tangent of elliptical shape Lissajous figure

y_1 is the distance from the origin to the point on y-axis, where the elliptical shape Lissajous figure intersects

y_2 is the distance from the origin to the horizontal tangent of elliptical shape Lissajous figure

SPECIAL PURPOSE OSCILLOSCOPE:


In previous chapter, we had discussed about Cathode Ray Oscilloscope (CRO), which is a basic oscilloscope. We will get special purpose oscilloscopes just by including few additional blocks to the basic oscilloscope based on the requirement.

Following are the **special purpose oscilloscopes**.

- Dual Beam Oscilloscope
- Dual Trace Oscilloscope
- Digital Storage Oscilloscope

Dual Trace Oscilloscope:

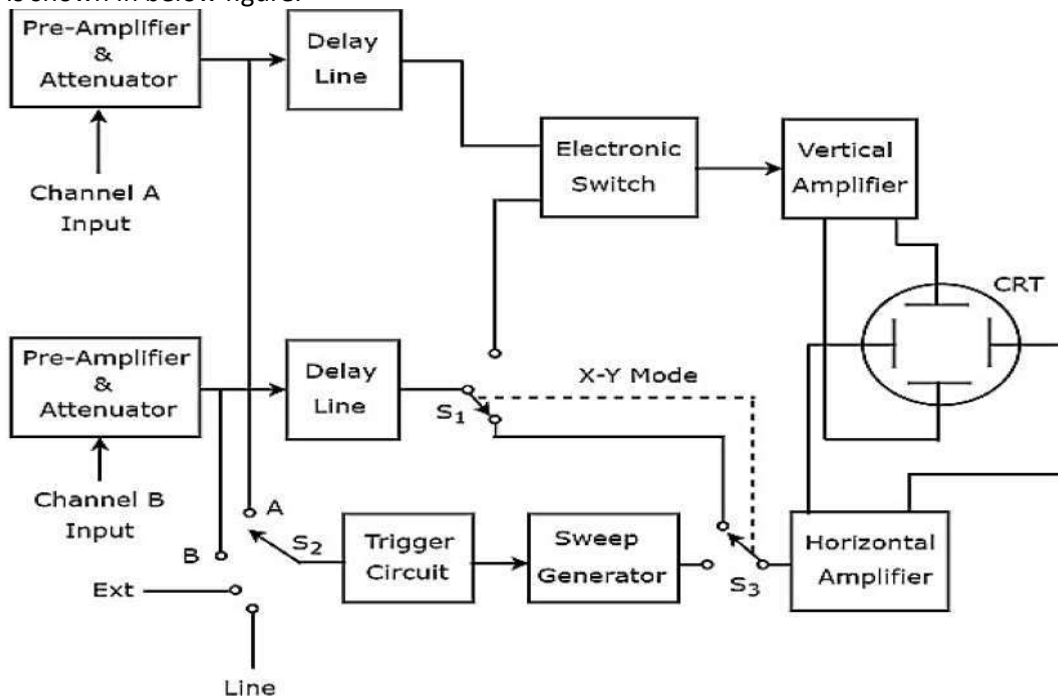The Oscilloscope, which produces two traces on its screen is called Dual Trace Oscilloscope. Its **block diagram** is shown in below figure.



As shown in above figure, the CRT of Dual Trace Oscilloscope consists of a set of vertical deflection plates and another set of horizontal deflection plates. **channel** consists of four blocks, i.e. pre-Amplifier & attenuator, delay line, vertical amplifier and vertical deflection plates.


In above block diagram, the first two blocks are separately present in both channels. The last two blocks are common to both the channels. Hence, with the help of **electronic switch** we can connect the delay line output of a specific channel to vertical amplifier.

We can choose any one of these four signals as **trigger input** to the trigger circuit by using a switch. Those are input signals A & B, External signal (Ext) and Line input.

This oscilloscope uses same electron beam for deflecting the input signals A & B in vertical direction by using an electronic switch, and produces **two traces**. the blocks that deflect the beam horizontally is common for both the input signals

Digital Storage Oscilloscope:

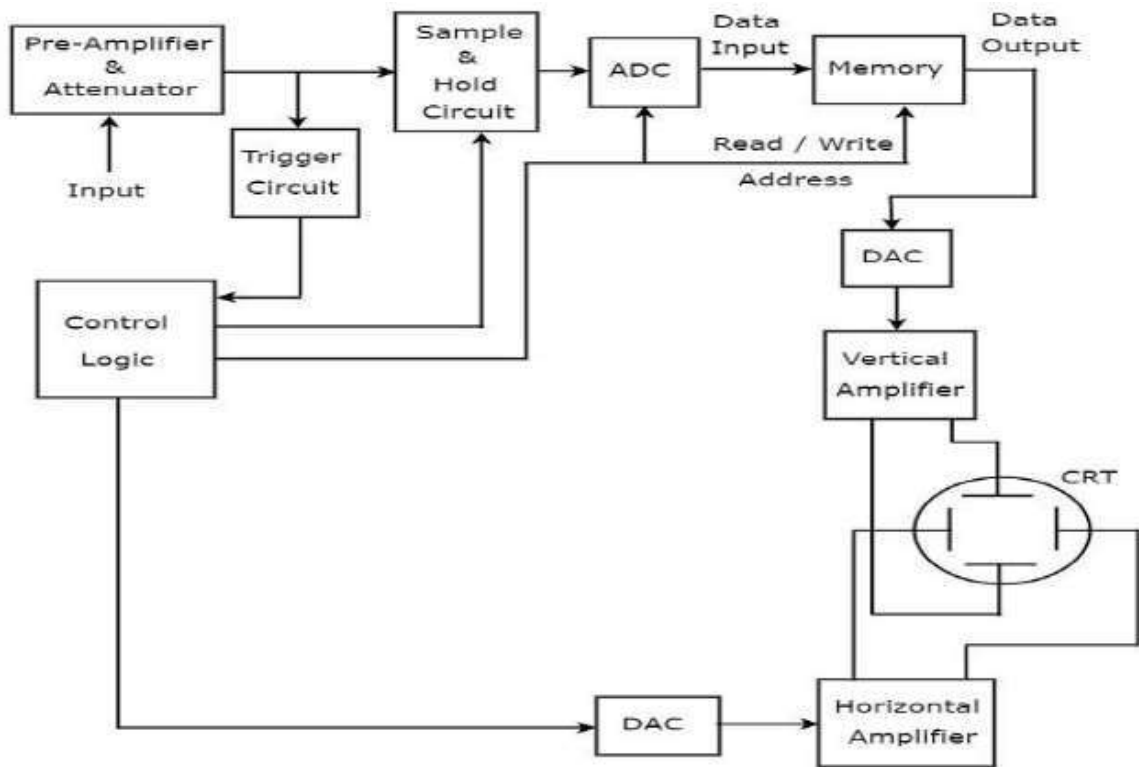The oscilloscope, which stores the waveform digitally is known as digital storage oscilloscope. The **block diagram** of (digital) storage oscilloscope is below:



Additional blocks required for digital data storage are added to a basic oscilloscope to make it convert it into a Digital Storage Oscilloscope. The blocks that are required for **storing of digital data** are lies between the pre-amplifier & attenuator and vertical amplifier in Digital Storage Oscilloscope. Those are Sample and Hold circuit, Analog to Digital Converter (ADC), Memory & Digital to Analog Converter.

Control logic controls the first three blocks by sending various control signals. The blocks like control logic and Digital to Analog Converter are present between the trigger circuit and horizontal amplifier in Digital Storage Oscilloscope.

The Digital Storage Oscilloscope **stores the data** in digital before it displays the waveform on the screen. Whereas, the basic oscilloscope doesn't have this feature.

UNIT- 5

BRIDGES

If the electrical components are arranged in the form a bridge or ring structure, then that electrical circuit is called a **bridge**. In general, bridge forms a loop with a set of four arms or branches. Each branch may contain one or two electrical components.

Types of Bridges:


We can classify the bridge circuits or bridges into the following two categories based on the voltage signal with which those can be operated.

- DC Bridges
- AC Bridges

Now, let us discuss about these two bridges briefly.

DC Bridges

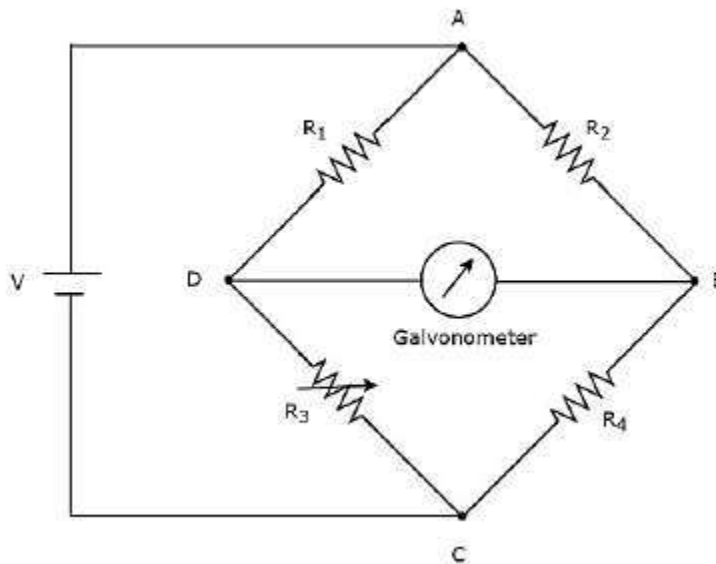If the bridge circuit can be operated with only DC voltage signal, then it is a DC bridge circuit or simply **DC bridge**. DC bridges are used to measure the value of unknown resistance. The **circuit diagram** of DC bridge looks like as shown in below figure.




The above DC bridge has **four arms** and each arm consists of a resistor. Among which, two resistors have fixed resistance values, one resistor is a variable resistor and the other one has an unknown resistance value.

The above DC bridge circuit can be excited with a **DC voltage source** by placing it in one diagonal. The galvanometer is placed in other diagonal of DC bridge. It shows some deflection as long as the bridge is unbalanced.

Vary the resistance value of variable resistor until the galvanometer shows null (zero) deflection. Now, the above DC bridge is said to be a balanced one. So, we can find the value of **unknown resistance** by using nodal equations.

AC Bridges :

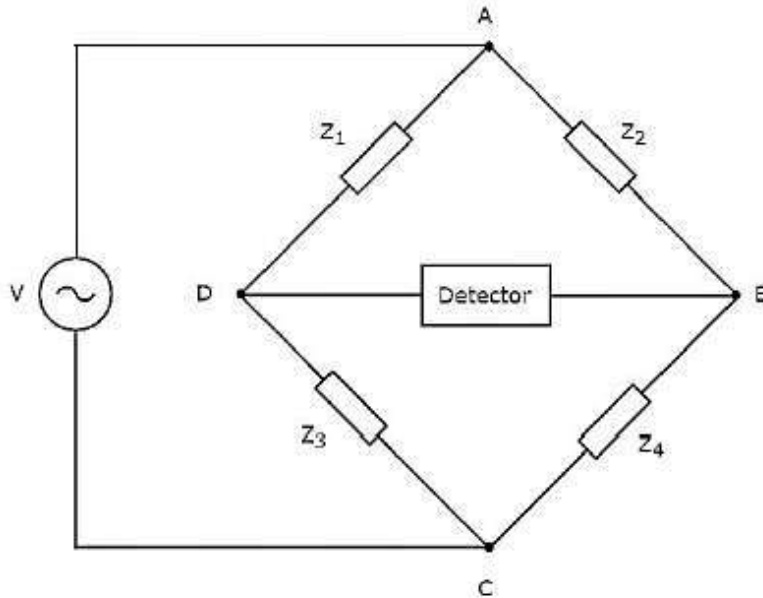If the bridge circuit can be operated with only AC voltage signal, then it is said to be AC bridge circuit or simply **AC bridge**. AC bridges are used to measure the value of unknown inductance, capacitance and frequency. The **circuit diagram** of AC bridge looks like as shown in below figure.



The circuit diagram of AC bridge is similar to that of DC bridge. The above AC bridge has **four arms** and each arm consists of some impedance. That means, each arm will be having either single or combination of passive elements such as resistor, inductor and capacitor.

Among the four impedances, two impedances have fixed values, one impedance is variable and the other one is an unknown impedance.

The above AC bridge circuit can be excited with an **AC voltage source** by placing it in one diagonal. A detector is placed in other diagonal of AC bridge. It shows some deflection as long as the bridge is unbalanced.


Vary the impedance value of variable impedance until the detector shows null (zero) deflection. Now, the above AC bridge is said to be a balanced one. So, we can find the value of **unknown impedance** by using balanced condition.

DC Bridges (Measurement of Resistance by Wheatstone's Bridge):

Wheatstone's bridge is a simple DC bridge, which is mainly having **four arms**. These four arms form a rhombus or square shape and each arm consists of one resistor.

To find the value of unknown resistance, we need the galvanometer and DC voltage source. Hence, one of these two are placed in one diagonal of Wheatstone's bridge and the other one is placed in another diagonal of Wheatstone's bridge.

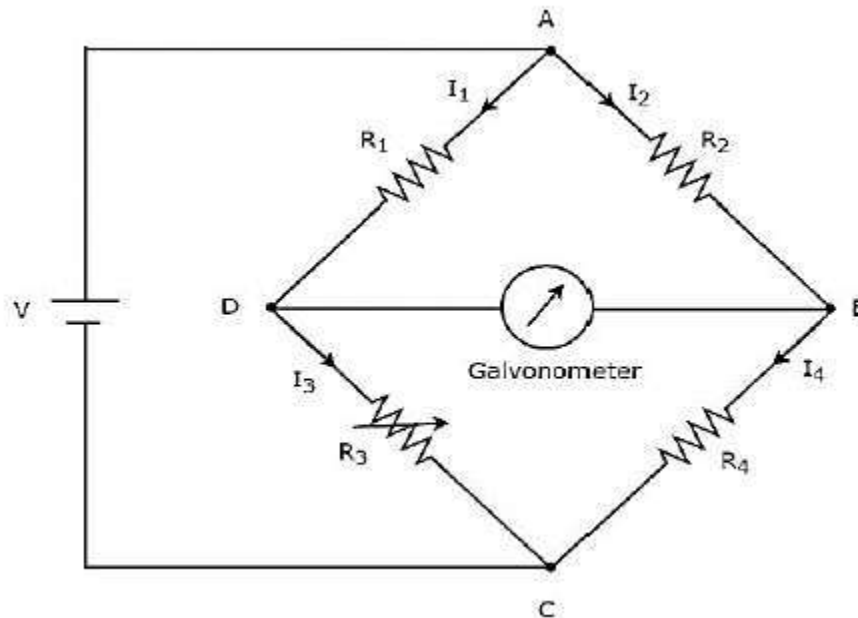Wheatstone's bridge is used to measure the value of medium resistance. The **circuit diagram** of Wheatstone's bridge is shown in below figure.



In above circuit, the arms AB, BC, CD and DA together form a **rhombus** or square shape. They consist of resistors R_2 , R_4 , R_3 and R_1 respectively. Let the current flowing through these resistor arms is I_2 , I_4 , I_3 and I_1 respectively and the directions of these currents are shown in the figure.

The diagonal arms DB and AC consists of galvanometer and DC voltage source of V volts respectively.

Here, the resistor, R_3 is a standard variable resistor and the

resistor, R_4 is an unknown resistor. We can **balance the bridge**, by varying the resistance value of resistor, R_3 .

The above bridge circuit is balanced when no current flows through the diagonal arm, DB. That means, there is **no deflection** in the galvanometer, when the bridge is balanced.

The bridge will be balanced, when the following **two conditions** are satisfied.

- The voltage across arm AD is equal to the voltage across arm AB.
i.e.,

$$V_{AD} = V_{AB}$$

$$\Rightarrow I_1 R_1 = I_2 R_2 \quad \text{Equation 1}$$

- The voltage across arm DC is equal to the voltage across arm BC.
i.e.,

$$V_{DC} = V_{BC}$$

$$\Rightarrow I_3 R_3 = I_4 R_4 \quad \text{Equation 2}$$

From above two balancing conditions, we will get the following **two conclusions**.

- The current flowing through the arm AD will be equal to that of arm DC. i.e.,

$$I_1 = I_3$$

- The current flowing through the arm AB will be equal to that of arm BC. i.e.,

$$I_2 = I_4$$

Take the ratio of Equation 1 and Equation 2.

$$\frac{I_1 R_1}{I_2 R_3} = \frac{I_2 R_2}{I_4 R_4} \quad \text{Equation 3}$$


Substitute, $I_1 = I_3$ and $I_2 = I_4$ in Equation 3.

$$\begin{aligned} \frac{I_3 R_1}{I_3 R_3} &= \frac{I_4 R_2}{I_4 R_4} \\ \Rightarrow \frac{R_1}{R_3} &= \frac{R_2}{R_4} \\ \Rightarrow R_4 &= \frac{R_2 R_3}{R_1} \end{aligned}$$

By substituting the known values of resistors R_1 , R_2 and R_3 in above equation, we will get the **value of resistor, R_4** .

AC bridges:

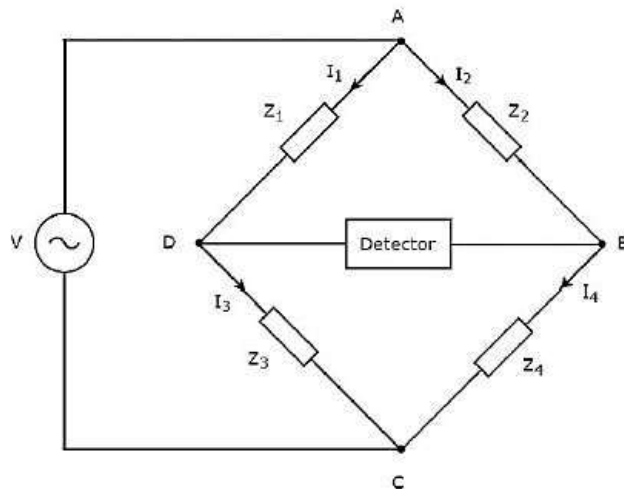In this chapter, let us discuss about the AC bridges, which can be used to measure inductance. AC bridges operate with only AC voltage signal. The **circuit diagram** of AC bridge is shown in below figure.



As shown in above figure, AC bridge mainly consists of four arms, which are connected in rhombus or **square shape**. All these arms consist of some impedance.

The detector and AC voltage source are also required in order to find the value of unknown impedance. Hence, one of these two are placed in one diagonal of AC bridge and the other one is placed in other diagonal of AC bridge. The balancing condition of Wheatstone's bridge as:

$$R_4 = \frac{R_2 R_3}{R_1}$$

We will get the **balancing condition of AC bridge**, just by replacing R with Z in above equation.

$$Z_4 = \frac{Z_2 Z_3}{Z_1}$$

$$\Rightarrow Z_1 Z_4 = Z_2 Z_3$$

Here, Z_1 and Z_2 are fixed impedances. Whereas, Z_3 is a standard variable impedance and Z_4 is an unknown impedance.

Note: We can choose any two of those four impedances as fixed impedances, one impedance as standard variable impedance & the other impedance as an unknown impedance based on the application.

Following are the two AC bridges, which can be used to measure **inductance**.

- Maxwell's Bridge
- Hay's Bridge


Now, let us discuss about these two AC bridges one by one.

Maxwell's Bridge:

Maxwell's bridge is an AC bridge having four arms, which are connected in the form of a rhombus or **square shape**. Two arms of this bridge consist of a single resistor, one arm consists of a series combination of resistor and inductor & the other arm consists of a parallel combination of resistor and capacitor.

An AC detector and AC voltage source are used to find the value of unknown impedance. Hence, one of these two are placed in one diagonal of Maxwell's bridge and the other one is placed in other diagonal of Maxwell's bridge.

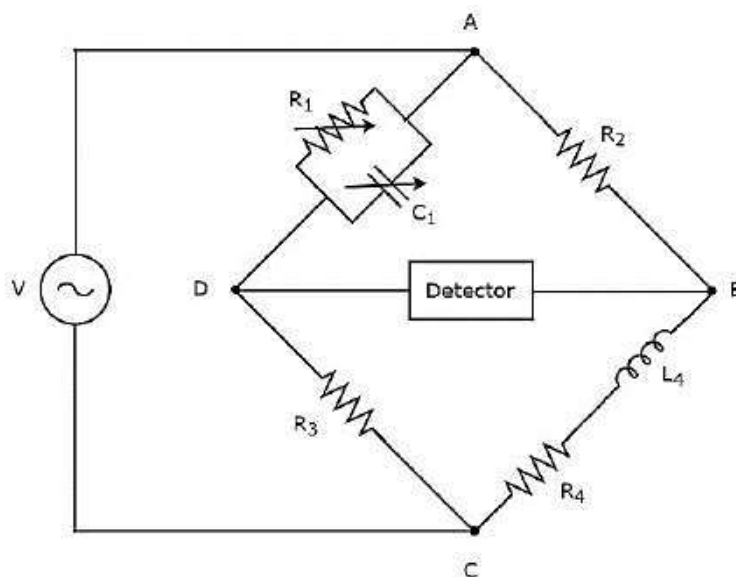Maxwell's bridge is used to measure the value of medium inductance. The **circuit diagram** of Maxwell's bridge is shown in the below figure.



In above circuit, the arms AB, BC, CD and DA together form a rhombus or square shape. The arms AB and CD consist of resistors, R_2 and R_3 respectively. The arm, BC

consists of a series combination of resistor, R_4 and inductor, L_4 . The arm, DA consists of a parallel combination of resistor, R_1 and capacitor, C_1 . Let, Z_1, Z_2, Z_3 and Z_4 are the impedances of arms DA, AB, CD and BC respectively. The **values of these impedances** will be

$$Z_1 = \frac{R_1 \left(\frac{1}{j\omega C_1} \right)}{R_1 + \frac{1}{j\omega C_1}}$$

$$\Rightarrow Z_1 = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 + j\omega L_4$$

Substitute these impedance values in the following balancing condition of AC bridge.

$$Z_4 = \frac{Z_2 Z_3}{Z_1}$$

$$R_4 + j\omega L_4 = \frac{R_2 R_3}{\left(\frac{R_1}{1 + j\omega R_1 C_1} \right)}$$

$$\Rightarrow R_4 + j\omega L_4 = \frac{R_2 R_3 (1 + j\omega R_1 C_1)}{R_1}$$

$$\Rightarrow R_4 + j\omega L_4 = \frac{R_2 R_3}{R_1} + \frac{j\omega R_1 C_1 R_2 R_3}{R_1}$$

$$\Rightarrow R_4 + j\omega L_4 = \frac{R_2 R_3}{R_1} + j\omega C_1 R_2 R_3$$

By **comparing** the respective real and imaginary terms of above equation, we will get

$$R_4 = \frac{R_2 R_3}{R_1} \quad \text{Equation 1}$$

$$L_4 = C_1 R_2 R_3 \quad \text{Equation 2}$$


By substituting the values of resistors R_1, R_2 and R_3 in Equation 1, we will get the value of resistor, R_4 . Similarly, by substituting the value of capacitor, C_1 and the values of resistors, R_2 and R_3 in Equation 2, we will get the value of inductor, L_4 .

The **advantage** of Maxwell's bridge is that both the values of resistor, R_4 and an inductor, L_4 are independent of the value of frequency.

Hay's Bridge:

Hay's bridge is a modified version of Maxwell's bridge, which we get by modifying the arm, which consists of a parallel combination of resistor and capacitor into the arm, which consists of a series combination of resistor and capacitor in Maxwell's bridge

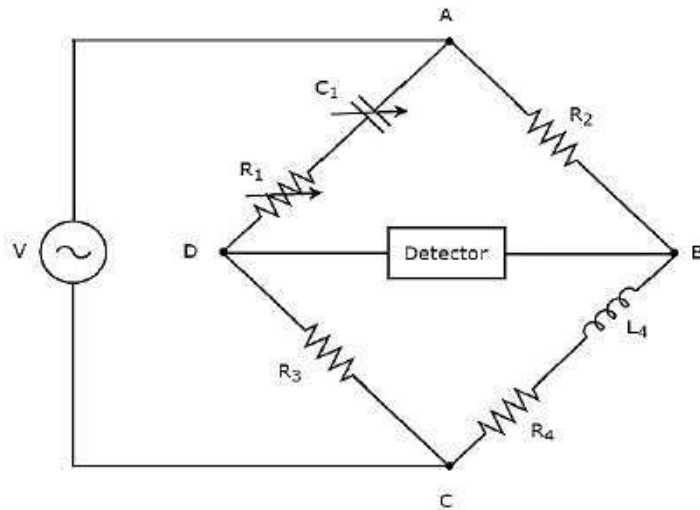Hay's bridge is used to measure the value of high inductance. The **circuit diagram** of Hay's bridge is shown in the below figure.



In above circuit, the arms AB, BC, CD and DA together form a rhombus or square shape. The arms, AB and CD consist of resistors, R_2 and R_3 respectively. The arm, BC consists of a series combination of resistor, R_4 and inductor, L_4 . The arm, DA consists of a series combination of resistor, R_1 and capacitor, C_1 .

Let, Z_1, Z_2, Z_3 and Z_4 are the impedances of arms DA, AB, CD and BC respectively. The **values of these impedances** will be

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$\Rightarrow Z_1 = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_2 = R_2$$

$$Z_3 = R_3$$

$$Z_4 = R_4 + j\omega L_4$$

Substitute these impedance values in the following balancing condition of AC bridge.

$$Z_4 = \frac{Z_2 Z_3}{Z_1}$$

$$R_4 + j\omega L_4 = \frac{R_2 R_3}{\left(\frac{1 + j\omega R_1 C_1}{j\omega C_1}\right)}$$

$$\Rightarrow R_4 + j\omega L_4 = \frac{R_2 R_3 j\omega C_1}{(1 + j\omega R_1 C_1)}$$

Multiply the numerator and denominator of right hand side term of above equation with $1 - j\omega R_1 C_1$.

$$\Rightarrow R_4 + j\omega L_4 = \frac{R_2 R_3 j\omega C_1}{(1 + j\omega R_1 C_1)} \times \frac{(1 - j\omega R_1 C_1)}{(1 - j\omega R_1 C_1)}$$

$$\Rightarrow R_4 + j\omega L_4 = \frac{\omega^2 C_1^2 R_1 R_2 R_3 + j\omega R_2 R_3 C_1}{(1 + \omega^2 R_1^2 C_1^2)}$$

By **comparing** the respective real and imaginary terms of above equation, we will get

$$R_4 = \frac{\omega^2 C_1^2 R_1 R_2 R_3}{(1 + \omega^2 R_1^2 C_1^2)} \quad \text{Equation 3}$$

$$L_4 = \frac{R_2 R_3 C_1}{(1 + \omega^2 R_1^2 C_1^2)} \quad \text{Equation 4}$$


By substituting the values of R_1, R_2, R_3, C_1 and ω in Equation 3 and Equation 4, we will get the values of resistor, R_4 and inductor, L_4 .

Measurement of capacitance by Schering's Bridge:

Schering bridge is an AC bridge having four arms, which are connected in the form of a rhombus or **square shape**, whose one arm consists of a single resistor, one arm consists of a series combination of resistor and capacitor, one arm consists of a single capacitor & the other arm consists of a parallel combination of resistor and capacitor.

The AC detector and AC voltage source are also used to find the value of unknown impedance, hence one of them is placed in one diagonal of Schering bridge and the other one is placed in other diagonal of Schering bridge.

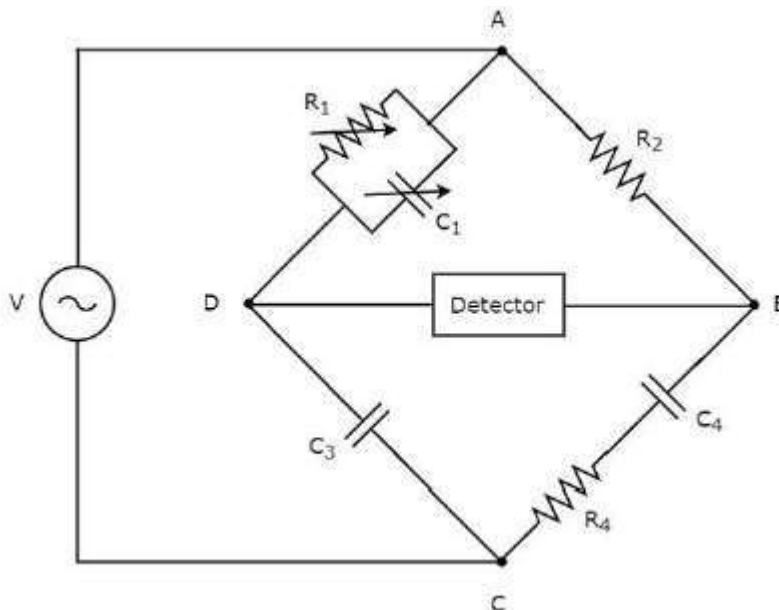Schering bridge is used to measure the value of capacitance. The **circuit diagram** of Schering bridge is shown in the below figure.



In above circuit, the arms AB, BC, CD and DA together form a rhombus or **square shape**. The arm AB consists of a resistor, R_2 . The arm BC consists of a series combination of resistor, R_4 and capacitor, C_4 . The arm CD consists of a capacitor, C_3 . The arm DA consists of a parallel combination of resistor, R_1 and capacitor, C_1 . Let, Z_1, Z_2, Z_3 and Z_4 are the impedances of arms DA, AB, CD and BC respectively. The **values of these impedances** will be

$$Z_1 = \frac{R_1 \left(\frac{1}{j\omega C_1} \right)}{R_1 + \frac{1}{j\omega C_1}}$$

$$\Rightarrow Z_1 = \frac{R_1}{1 + j\omega R_1 C_1}$$

$$Z_2 = R_2$$

$$Z_3 = \frac{1}{j\omega C_3}$$

$$Z_4 = R_4 + \frac{1}{j\omega C_4}$$

$$\Rightarrow Z_4 = \frac{1 + j\omega R_4 C_4}{j\omega C_4}$$

Substitute these impedance values in the following balancing condition of AC bridge.

$$Z_4 = \frac{Z_2 Z_3}{Z_1}$$

$$\frac{1 + j\omega R_4 C_4}{j\omega C_4} = \frac{R_2 \left(\frac{1}{j\omega C_3} \right)}{1 + j\omega R_1 C_1}$$

$$\Rightarrow \frac{1 + j\omega R_4 C_4}{j\omega C_4} = \frac{R_2 (1 + j\omega R_1 C_1)}{j\omega R_1 C_3}$$

$$\Rightarrow \frac{1 + j\omega R_4 C_4}{C_4} = \frac{R_2 (1 + j\omega R_1 C_1)}{R_1 C_3}$$

$$\Rightarrow \frac{1}{C_4} + j\omega R_4 = \frac{R_2}{R_1 C_3} + \frac{j\omega C_1 R_2}{C_3}$$

By **comparing** the respective real and imaginary terms of above equation, we will get

$$C_4 = \frac{R_1 C_3}{R_2} \quad \text{Equation 1}$$

$$R_4 = \frac{C_1 R_2}{C_3} \quad \text{Equation 2}$$

By substituting the values of R_1, R_2 and C_3 in Equation 1, we will get the value of capacitor, C_4 . Similarly, by substituting the values of R_2, C_1 and C_3 in Equation 2, we will get the value of resistor, R_4 .


The advantage of Schering bridge is that both the values of resistor, R_4 and capacitor, C_4 are independent of the value of frequency.

Measurement of frequency(Wien's Bridge)

Wien's bridge is an AC bridge having four arms, which are connected in the form of a rhombus or square shape. Among two arms consist of a single resistor, one arm consists of a parallel combination of resistor and capacitor & the other arm consists of a series combination of resistor and capacitor.

The AC detector and AC voltage source are also required in order to find the value of frequency. Hence, one of these two are placed in one diagonal of Wien's bridge and the other one is placed in other diagonal of Wien's bridge.

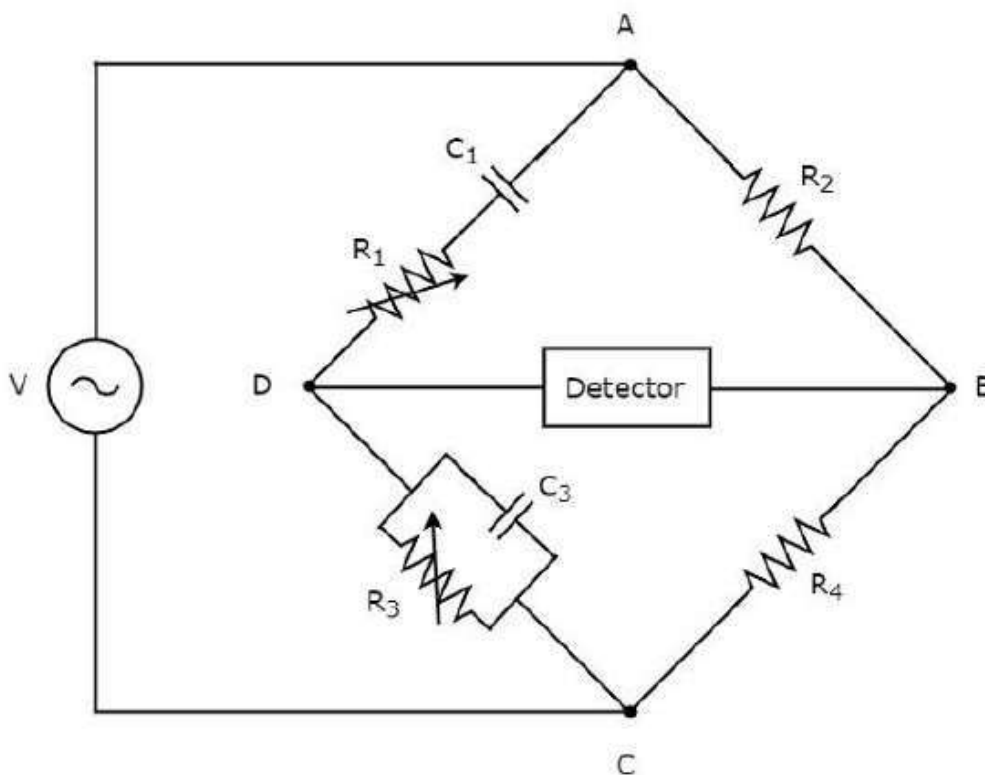The **circuit diagram** of Wien's bridge is shown in the below figure



In above circuit, the arms AB, BC, CD and DA together form a rhombus or **square shape**. The arms, AB and BC consist of resistors, R_2 and R_4 respectively. The arm, CD consists of a parallel combination of resistor, R_3 and capacitor, C_3 . The arm, DA consists of a series combination of resistor, R_1 and capacitor, C_1 .

Let, Z_1 , Z_2 , Z_3 and Z_4 are the impedances of arms DA, AB, CD and BC respectively. The **values of these impedances** will be

$$Z_1 = R_1 + \frac{1}{j\omega C_1}$$

$$\Rightarrow Z_1 = \frac{1 + j\omega R_1 C_1}{j\omega C_1}$$

$$Z_2 = R_2$$

$$Z_3 = \frac{R_3 \left(\frac{1}{j\omega C_3} \right)}{R_3 + \frac{1}{j\omega C_3}}$$

$$\Rightarrow Z_3 = \frac{R_3}{1 + j\omega R_3 C_3}$$

$$Z_4 = R_4$$

Substitute these impedance values in the following balancing condition of AC bridge.

$$Z_1 Z_4 = Z_2 Z_3$$

$$\left(\frac{1 + j\omega R_1 C_1}{j\omega C_1} \right) R_4 = R_2 \left(\frac{R_3}{1 + j\omega R_3 C_3} \right)$$

$$\Rightarrow (1 + j\omega R_1 C_1)(1 + j\omega R_3 C_3) R_4 = j\omega C_1 R_2 R_3$$

$$\Rightarrow (1 + j\omega R_3 C_3 + j\omega R_1 C_1 - \omega^2 R_1 R_3 C_1 C_3) R_4 = j\omega C_1 R_2 R_3$$

$$\Rightarrow R_4 (1 - \omega^2 R_1 R_3 C_1 C_3) + j\omega R_4 (R_3 C_3 + R_1 C_1) = j\omega C_1 R_2 R_3$$

Equate the respective **real terms** of above equation.

$$R_4 (1 - \omega^2 R_1 R_3 C_1 C_3) = 0$$

$$\Rightarrow 1 - \omega^2 R_1 R_3 C_1 C_3 = 0$$

$$\Rightarrow 1 = \omega^2 R_1 R_3 C_1 C_3$$

$$\Rightarrow \omega^2 = \frac{1}{R_1 R_3 C_1 C_3}$$

$$\Rightarrow \omega = \frac{1}{\sqrt{R_1 R_3 C_1 C_3}}$$


We can find the value of frequency, f of AC voltage source by substituting the values of R_1 , R_3 , C_1 and C_3 in above equation.

If $R_1=R_3=R$ and $C_1=C_3=C$, then we can find the value of frequency, f of AC voltage source by using the following formula. $f=1/2\pi RC$

The Wein's bridge is mainly used for finding the **frequency value** of AF range.

UNIT- 6
TRANSDUCER & SENSORS

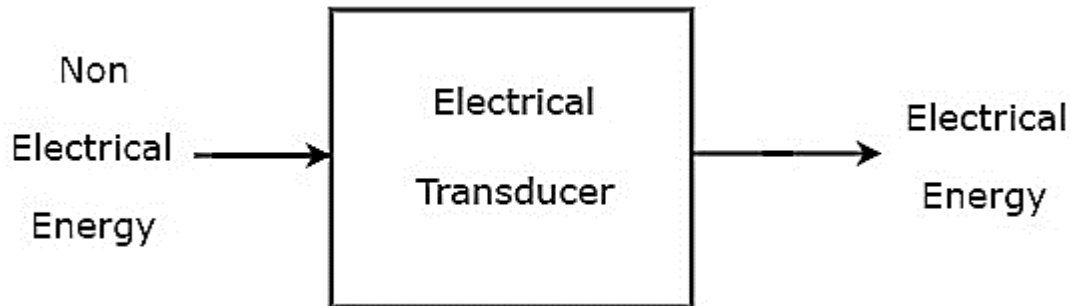Basically, Transducer converts one form of energy into another form of energy. The transducer, which converts non-electrical form of energy into electrical form of energy is known as **electrical transducer**. The **block diagram** of electrical transducer is shown in below figure.



As shown in the figure, electrical transducer will produce an output, which has electrical energy. The output of electrical transducer is equivalent to the input, which has non-electrical energy.

Types of Electrical Transducers:

Mainly, the electrical transducers can be classified into the following **two types**.


- Active Transducers

- Passive Transducers

ACTIVE TRANSDUCERS

The transducer which can produce one of the electrical quantities such as voltage and current is known as **Active Transducer**. It is also called **self generating Transducer** since it does not require any external Power supply.

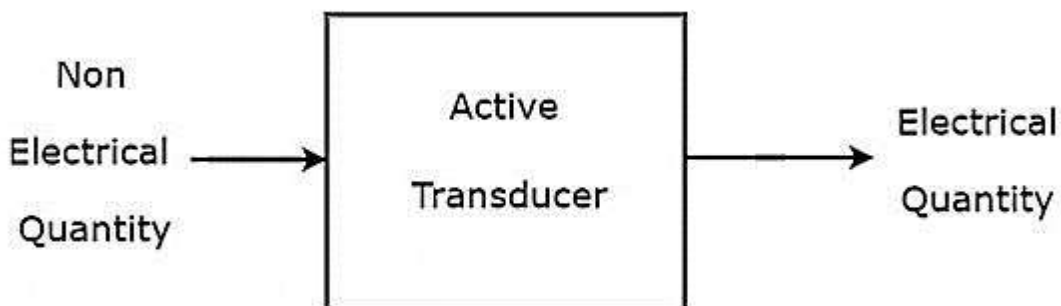The block diagram of Active transducer as shown below.



As shown in the figure, active transducer will produce an electrical quantity (or signal), which is equivalent to the non-electrical input quantity (or signal).

Examples

Following are the examples of active transducers.

- ☒ Piezo Electric Transducer
- ☒ Photo Electric Transducer
- ☒ Thermo Electric Transducer

Resistive Transducer :

A passive transducer is said to be a **resistive transducer**, when it produces the variation (change) in resistance value. the following formula for **resistance**, R of a metal conductor.

$$R = \rho l / A$$

Where,

ρ is the resistivity of conductor

l is the length of conductor

A is the cross sectional area of the conductor


The resistance value depends on the three parameters ρ , l & A . So, we can make the **resistive transducers** based on the variation in one of the three parameters ρ , l & A . The variation in any one of those three parameters changes the resistance value.

- Resistance, R is directly proportional to the **resistivity** of conductor, ρ . So, as resistivity of conductor, ρ increases the value of resistance, R also increases. Similarly, as resistivity of conductor, ρ decreases the value of resistance, R also decreases.
- Resistance, R is directly proportional to the **length** of conductor, l . So, as length of conductor, l increases the value of resistance, R also increases. Similarly, as length of conductor, l decreases the value of resistance, R also decreases.
- Resistance, R is inversely proportional to the **cross sectional area** of the conductor, A . So, as cross sectional area of the conductor, A increases the value of resistance, R decreases. Similarly, as cross sectional area of the conductor, A decreases the value of resistance, R increases.

Strain Gauge Measurement:

What is Strain?

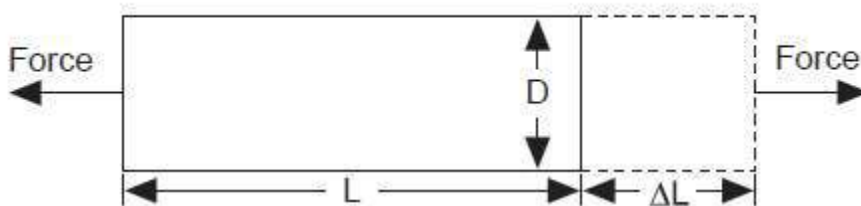Strain is the amount of deformation of a body due to an applied force. More specifically, strain (ϵ) is defined as the fractional change in length, as shown in Figure 1 below.



$$\epsilon = \frac{\Delta L}{L}$$

Figure 1. Definition of Strain

Strain can be positive (tensile) or negative (compressive). Although dimensionless, strain is sometimes expressed in units such as in./in. or mm/mm. In practice, the magnitude of measured strain is very small. Therefore, strain is often expressed as microstrain ($\mu\epsilon$), which is $\epsilon \times 10^{-6}$.

When a bar is strained with a uniaxial force, as in Figure 1, a phenomenon known as Poisson Strain causes the girth of the bar, D , to contract in the transverse, or perpendicular, direction. The magnitude of this transverse contraction is a

material property indicated by its Poisson's Ratio. The Poisson's Ratio ν of a material is defined as the negative ratio of the strain in the transverse direction (perpendicular to the force) to the strain in the axial direction (parallel to the force), or $\nu = -\epsilon_T/\epsilon$. Poisson's Ratio for steel, for example, ranges from 0.25 to 0.3.

Working Principle of Strain Gauge:

While there are several methods of measuring strain, the most common is with a strain gauge, a device whose electrical resistance varies in proportion to the amount of strain in the device. For example, the piezo resistive strain gauge is a semiconductor device whose resistance varies nonlinearly with strain. The most widely used gauge, however, is the bonded metallic strain gauge.

The metallic strain gauge consists of a very fine wire or, more commonly, metallic foil arranged in a grid pattern. The grid pattern maximizes the amount of metallic wire or foil subject to strain in the parallel direction (Figure 2). The cross sectional area of the grid is minimized to reduce the effect of shear strain and Poisson Strain. The grid is bonded to a thin backing, called the carrier, which is attached directly to the test specimen. Therefore, the strain experienced by the test specimen is transferred directly to the strain gauge, which responds with a linear change in electrical resistance. Strain gauges are available commercially with nominal resistance values from 30 to 3000 Ω , with 120, 350, and 1000 Ω being the most common values.

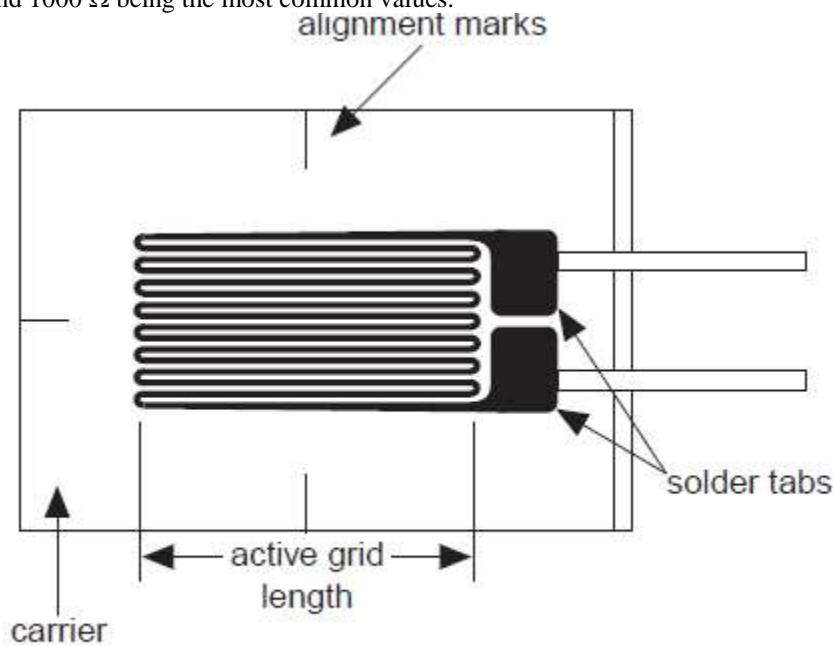


Figure 2. Bonded Metallic Strain Gauge

It is very important that the strain gauge be properly mounted onto the test specimen so that the strain is accurately transferred from the test specimen, through the adhesive and strain gauge backing, to the foil itself. Manufacturers of strain gauges are the best source of information on proper mounting of strain gauges.

A fundamental parameter of the strain gauge is its sensitivity to strain, expressed quantitatively as the gauge factor (GF). Gauge factor is defined as the ratio of fractional change in electrical resistance to the fractional change in length (strain):


$$GF = \frac{\Delta R/R}{\Delta L/L} = \frac{\Delta R/R}{\epsilon}$$

The Gauge Factor for metallic strain gauges is typically around 2.

Working principle of LVDT: (Linear variable differential Transformer)

Measurement of Displacement using Inductive Transducer:

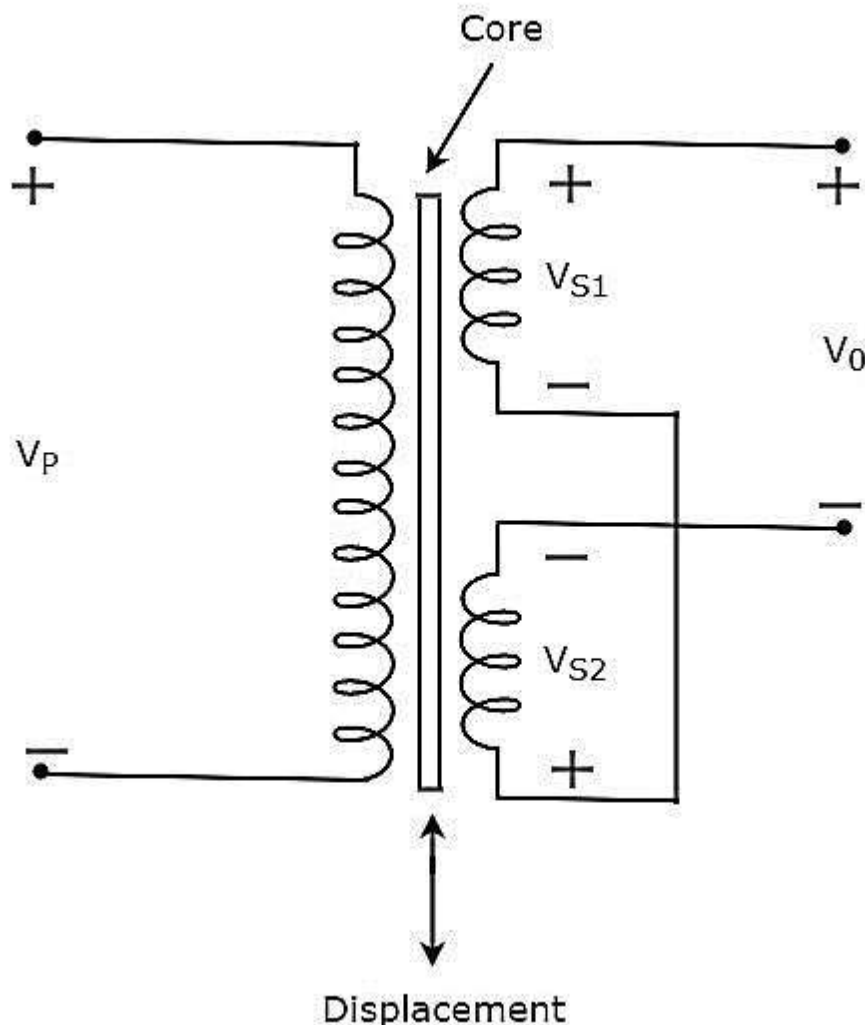The **circuit diagram** of inductive transducer, which is used to measure displacement is shown in below figure.



The transformer present in above circuit has a primary winding and two secondary windings. Here, the ending points of two secondary windings are joined together. So, we can say that these two secondary windings are connected in **series opposition**.

The voltage, V_P is applied across the primary winding of transformer. Let, the voltage developed across each secondary winding is V_{S1} and V_{S2} . The output voltage, V_0 is taken across the starting points of two secondary windings.

Mathematically, the output voltage, V_0 can be written as $V_0 = V_{S1} - V_{S2}$

The transformer present in above circuit is called **differential transformer**, since it produces an output voltage, which is the difference between V_{S1} and V_{S2} .


- If the core is at central position, then the output voltage, V_0 will be equal to zero. Because, the respective magnitudes & phases of V_{S1} and V_{S2} are same.

- If the core is not at central position, then the output voltage, V_0 will be having some magnitude & phase. Because, the respective magnitudes & phases of V_{S1} and V_{S2} are not equal. Therefore, we should connect the body whose displacement is to be measured to the central core. So, whenever the body moves in a straight line, the central position of the core varies. Due to this, the output voltage, V_0 also changes accordingly.

In this case, we can find the **displacement** by measuring the output voltage, V_0 . The magnitude & phase of output voltage, V_0 represents the displacement of the body & its direction respectively.

Measurement of Displacement using Capacitive Transducer:

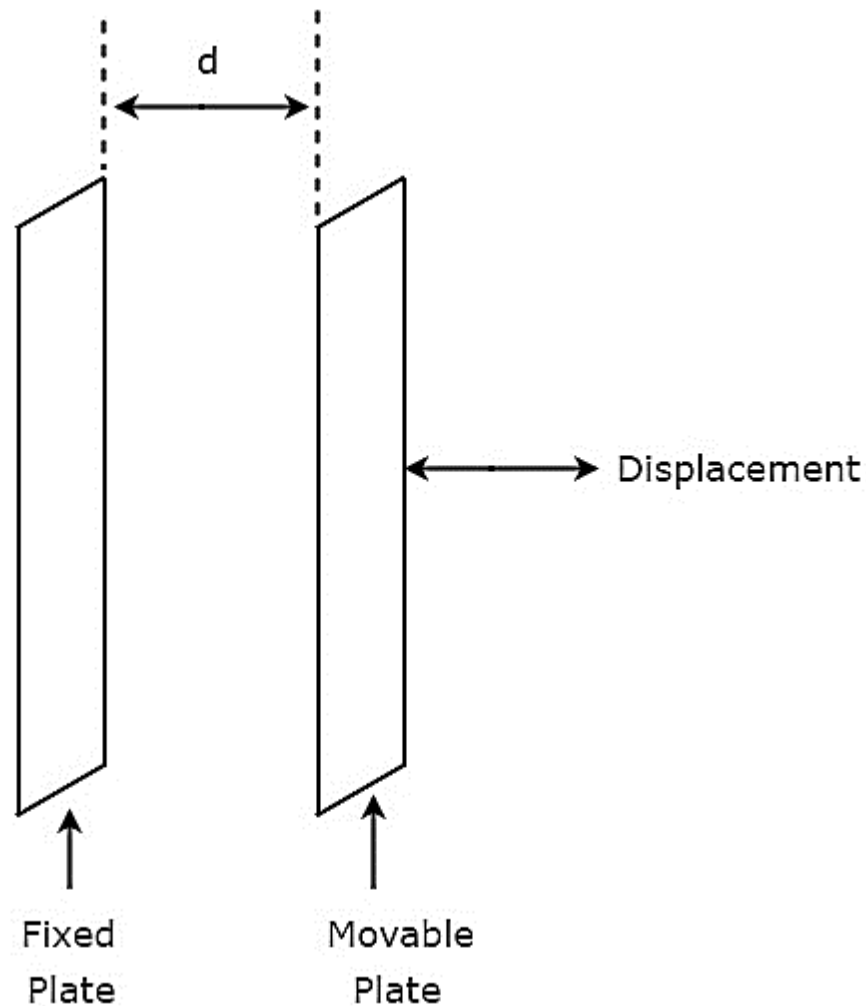The **circuit diagram** of capacitive transducer, which is used to measure displacement is shown in below figure.



The **capacitor**, which is present in above circuit has two parallel plates. Among which, one plate is fixed and the other plate is a movable one. Due to this, the spacing between these two plates will also vary. the value of capacitance changes as the spacing between two plates of capacitor changes.

Therefore, we should connect the body whose **displacement** is to be measured to the movable plate of a capacitor. So, whenever the body moves in a straight line, the spacing between the two plates of capacitor varies. Due to this, the capacitance value changes.

A passive transducer is said to be a **capacitive transducer**, when it produces the variation (change) in capacitance value. the following formula for **capacitance**, C of a parallel plate capacitor.

$$C = \epsilon A / d$$

Where,

ϵ is the permittivity or the dielectric constant

A is the effective area of two plates

d is the distance between two plates

The capacitance value depends on the three parameters ϵ , A & d . So, we can make the **capacitive transducers** based on the variation in one of the three parameters ϵ , A & d . Because, the variation in any one of those three parameters changes the capacitance value.

- Capacitance, C is directly proportional to **permittivity**, ϵ . So, as permittivity, ϵ increases the value of capacitance, C also increases. Similarly, as permittivity, ϵ decreases the value of capacitance, C also decreases.
- Capacitance, C is directly proportional to the **effective area of two plates**, A . So, as effective area of two plates, A increases the value of capacitance, C also increases. Similarly, as effective area of two plates, A decreases the value of capacitance, C also decreases.
- Capacitance, C is inversely proportional to the **distance between two plates**, d . So, as distance between two plates, d increases the value of capacitance, C decreases. Similarly, as distance between two plates, d decreases the value of capacitance, C increases.

Working principle of Temperature Transducer:

Thermistor Transducer:

The resistor, which depends on temperature is called thermal resistor. In short, it is called **Thermistor**. The temperature coefficient of thermistor is negative. That means, as temperature increases, the resistance of thermistor decreases.

Mathematically, the relation between resistance of thermistor and temperature can be represented as

$$R_1 = R_2 e^{\left(\beta \left[\frac{1}{T_1} - \frac{1}{T_2}\right]\right)}$$

Where,

R_1 is the resistance of thermistor at temperature T_1 K


R_2 is the resistance of thermistor at temperature T_2 K

β is the temperature constant

The advantage of Thermistor transducer is that it will produce a fast and stable response.

Thermocouple Transducer:

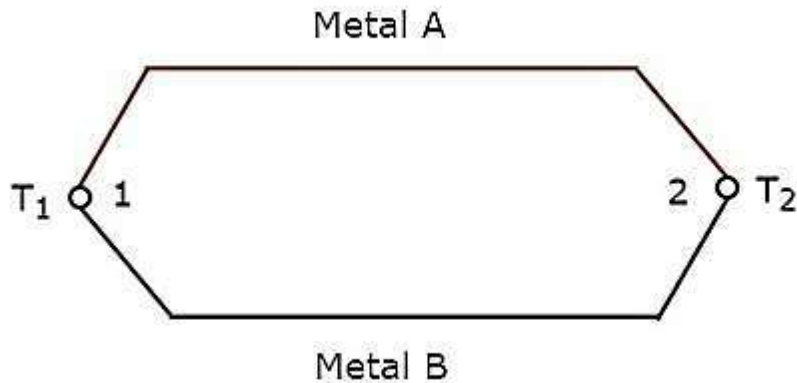Thermocouple transducer produces an output voltage for a corresponding change of temperature at the input. If two wires of different metals are joined together in order to create two junctions, then that entire configuration is called **Thermocouple**. The circuit diagram of basic thermocouple is shown below:



The above thermocouple has two metals, A & B and two junctions, 1 & 2. Consider a constant reference temperature, T_2 at junction 2. Let the temperature at junction, 1 is T_1 . Thermocouple generates an **emf** (electro motive force), whenever the values of T_1 and T_2 are different.


That means, thermocouple generates an emf, whenever there is a temperature difference between the two junctions, 1 & 2 and it is directly proportional to the temperature difference between those two junctions. **Mathematically**, it can be represented as

$$e \propto (T_1 - T_2)$$

Where,

e is the emf generated by thermocouple

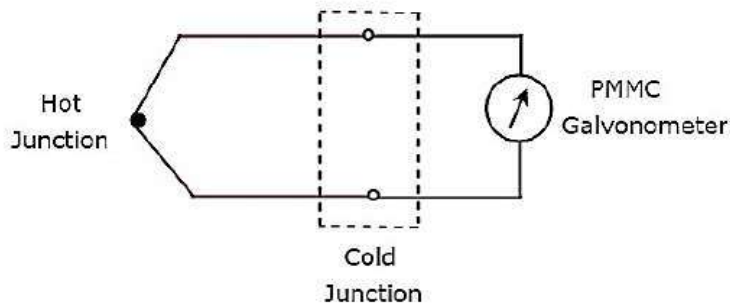The above thermocouple circuit can be represented as shown in below figure for practical applications.




The part of the circuit, which lies between hot & cold junctions including those two junctions is an equivalent model of basic thermocouple. A PMMC galvanometer is connected across the cold junction and it deflects according to the emf generated across cold junction. **Thermocouple transducer** is the most commonly used thermoelectric transducer.

Signal generator is an electronic equipment that provides standard test signals like sine wave, square wave, triangular wave and etc. It is also called an oscillator, since it produces periodic signals.

The signal generator, which produces the periodic signal having a frequency of Audio Frequency (AF) range is called **AF signal generator**. the range of audio frequencies is 20Hz to 20KHz.

AF Sine and Square Wave Generator:

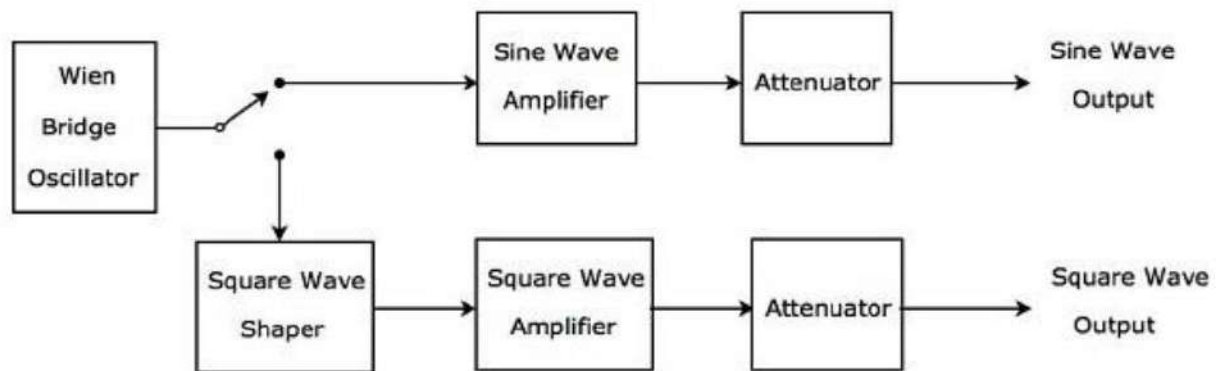The AF signal generator, which generates either sine wave or square wave in the range of audio frequencies based on the requirement is called AF Sine and Square wave generator. Its **block diagram** is shown in below figure.



The above block diagram consists of mainly **two paths**. Those are upper path and lower path. Upper path is used to produce AF sine wave and the lower path is used to produce AF square wave.


Wien bridge oscillator will produce a sine wave in the range of audio frequencies. Based on the requirement, we can connect the output of Wien bridge oscillator to either upper path or lower path by a switch.

The upper path consists of the blocks like sine wave amplifier and attenuator. If the switch is used to connect the output of Wien bridge oscillator to upper path, it will produce a desired **AF sine wave** at the output of upper path.

The lower path consists of the following blocks: square wave shaper, square wave amplifier, and attenuator. The square wave shaper converts the sine wave into a square wave. If the switch is used to connect the output of Wien bridge oscillator to lower path, then it will produce a desired **AF square wave** at the output of lower path. In this way, the block diagram that we considered can be used to produce either AF sine wave or AF square wave based on the requirement.

Working Principle of Function Generator:

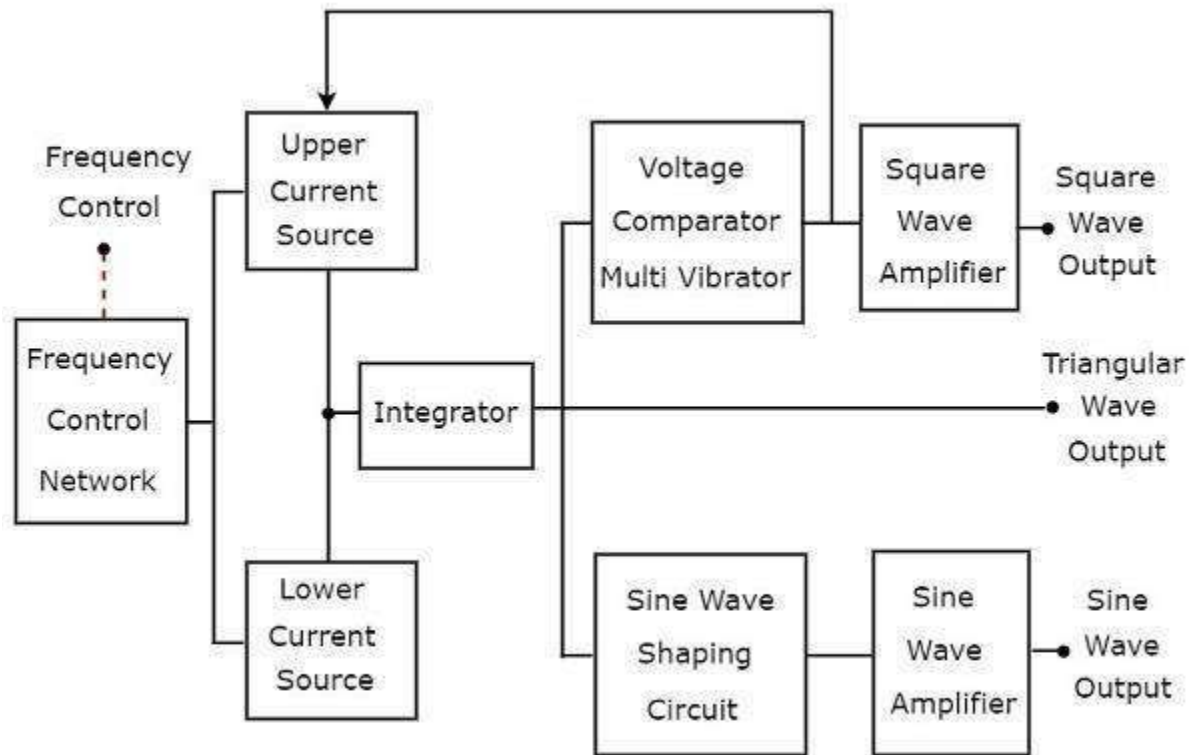Function generator is a signal generator, which generates three or more periodic waves. Consider the following **block diagram** of a Function generator, which will produce periodic waves like triangular wave, square wave and sine wave.



There are two **current sources**, namely upper current source and lower current source in above block diagram. These two current sources are regulated by the frequency-controlled voltage.

Triangular Wave:

Integrator present in the above block diagram, gets constant current alternately from upper and lower current sources for equal amount of time repeatedly. So, the integrator will produce two types of output for the same time repeatedly:

- The output voltage of an integrator **increases linearly** with respect to time for the period during which integrator gets current from upper current source.
 - The output voltage of an integrator **decreases linearly** with respect to time for the period during which integrator gets current from lower current source.
- In this way, the integrator present in above block diagram will produce a **triangular wave**.

Square Wave & Sine Wave:

The output of integrator, i.e. the triangular wave is applied as an input to two other blocks as shown in above block diagram in order to get the square wave and sine wave respectively. Let us discuss about these two one by one.

Square Wave:

The triangular wave has positive slope and negative slope alternately for equal amount of time repeatedly. So, the **voltage comparator multi vibrator** present in above block diagram will produce the following two types of output for equal amount of time repeatedly.

- One type of constant (**higher**) **voltage** at the output of voltage comparator multi vibrator for the period during which the voltage comparator multi vibrator gets the positive slope of the triangular wave.

- Another type of constant (**lower**) **voltage** at the output of voltage comparator multi vibrator for the period during which the voltage comparator multi vibrator gets the negative slope of the triangular wave.

The voltage comparator multi vibrator present in above block diagram will produce a **square wave**. If the amplitude of the square wave that is produced at the output of voltage comparator multi vibrator is not sufficient, then it can be amplified to the required value by using a square wave amplifier.

Sine Wave

The **sine wave shaping circuit** will produce a sine wave output from the triangular input wave. Basically, this circuit consists of a diode resistance network. If the amplitude of the sine wave produced at the output of sine wave shaping circuit is insufficient, then it can be amplified to the required value by using sine wave amplifier.

WAVE ANALYZERS

The electronic instrument used to analyze waves is called **wave analyzer**. It is also called signal analyzer, since the terms signal and wave can be interchangeably used frequently.


We can represent the **periodic signal** as sum of the following two terms.

- DC component
- Series of sinusoidal harmonics

So, analyzation of a periodic signal is analyzation of the harmonics components presents in it.

Basic Wave Analyzer:

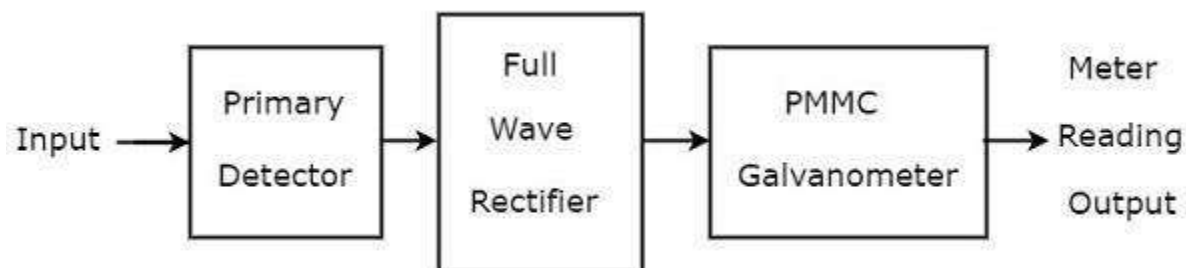Basic wave analyzer mainly consists of three blocks: the primary detector, full wave rectifier, and PMMC galvanometer. The **block diagram** of basic wave analyzer is shown in below figure:




The **function** of each block present in basic wave analyzer is mentioned below.

- **Primary Detector:** It consists of an LC circuit. We can adjust the values of inductor, L and capacitor, C in such a way that it allows only the desired harmonic frequency component that is to be measured.

- **Full Wave Rectifier:** It converts the AC input into a DC output

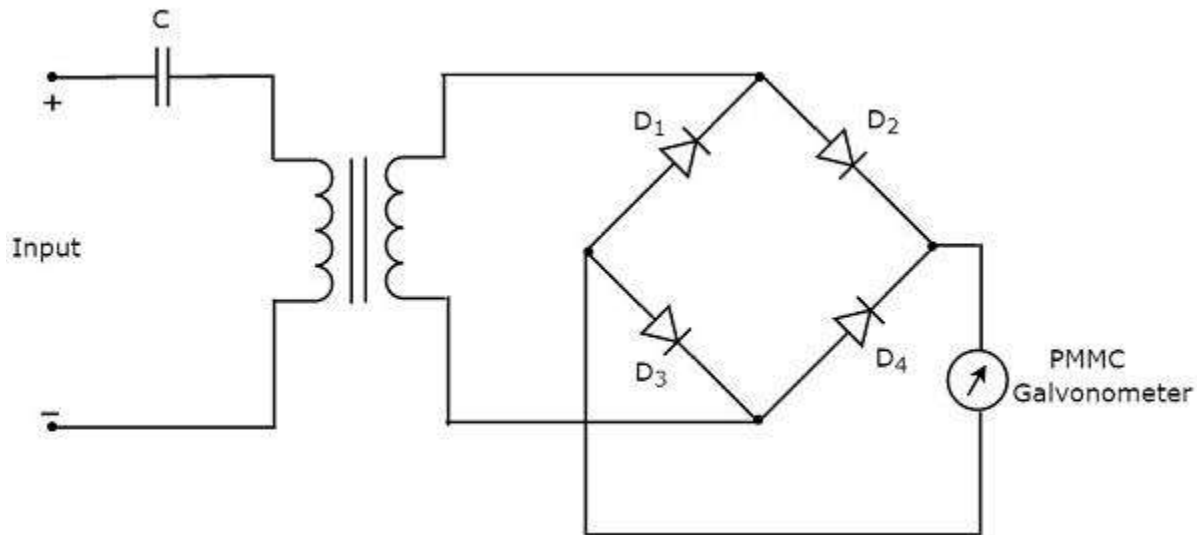- **PMMC Galvanometer:** It shows the peak value of the signal, which is obtained at the output of Full wave rectifier.



This basic wave analyzer can be used for analyzing each and every harmonic frequency component of a periodic signal.

SPECTRUM ANALYZER:

The electronic instrument, used for analyzing waves in frequency domain is called **spectrum analyzer**. Basically, it displays the energy distribution of a signal on its CRT screen. Here, x-axis represents frequency and y-axis represents the amplitude.

Types of Spectrum Analyzers:


We can classify the spectrum analyzers into the following **two types**.

- Filter bank spectrum analyzer
- Superheterodyne Spectrum analyzer

Filter Bank Spectrum Analyzer:

The spectrum analyzer, used for analyzing the signals are of AF range is called filter bank spectrum analyzer, or **real time spectrum analyzer** because it shows (displays) any variations in all input frequencies.

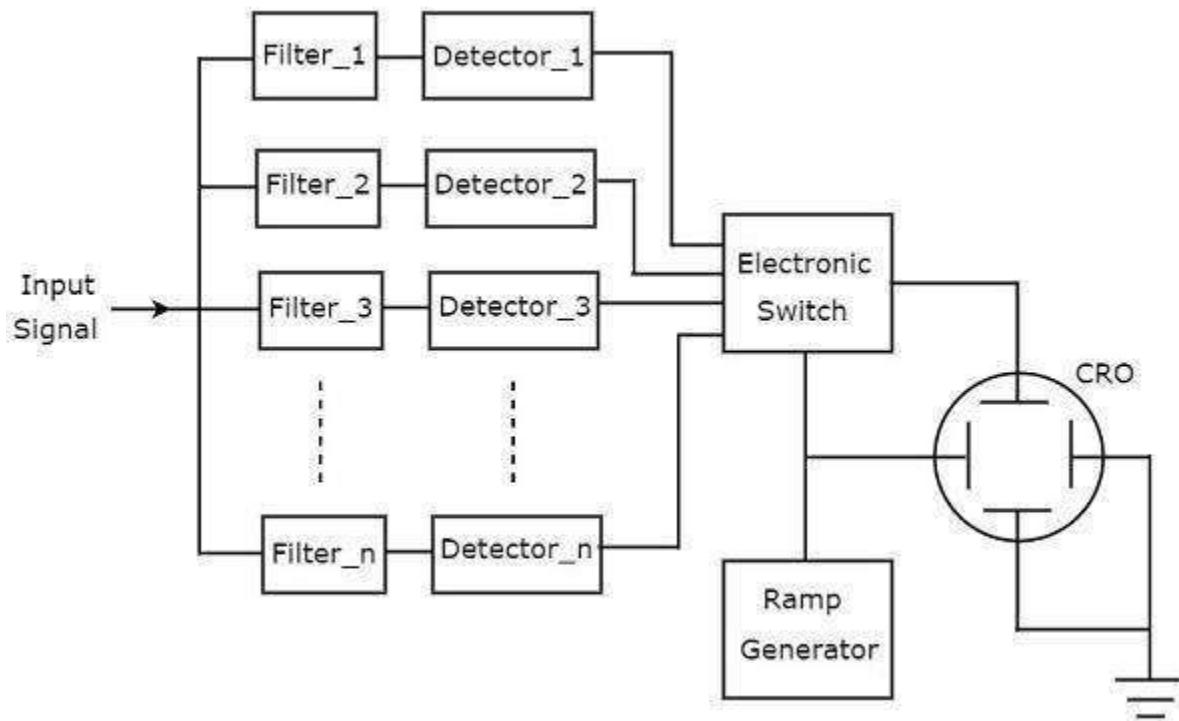The following figure shows the **block diagram** of filter bank spectrum analyzer.




The **working** of filter bank spectrum analyzer is mentioned below.

□ It has a set of band pass filters and each one is designed for allowing a specific band of frequencies. The output of each band pass filter is given to a corresponding detector.

• All the detector outputs are connected to Electronic switch. This switch allows the detector outputs sequentially to the vertical deflection plate of CRO. So, CRO displays the frequency **spectrum of AF signal** on its CRT screen.

Superheterodyne Spectrum Analyzer:

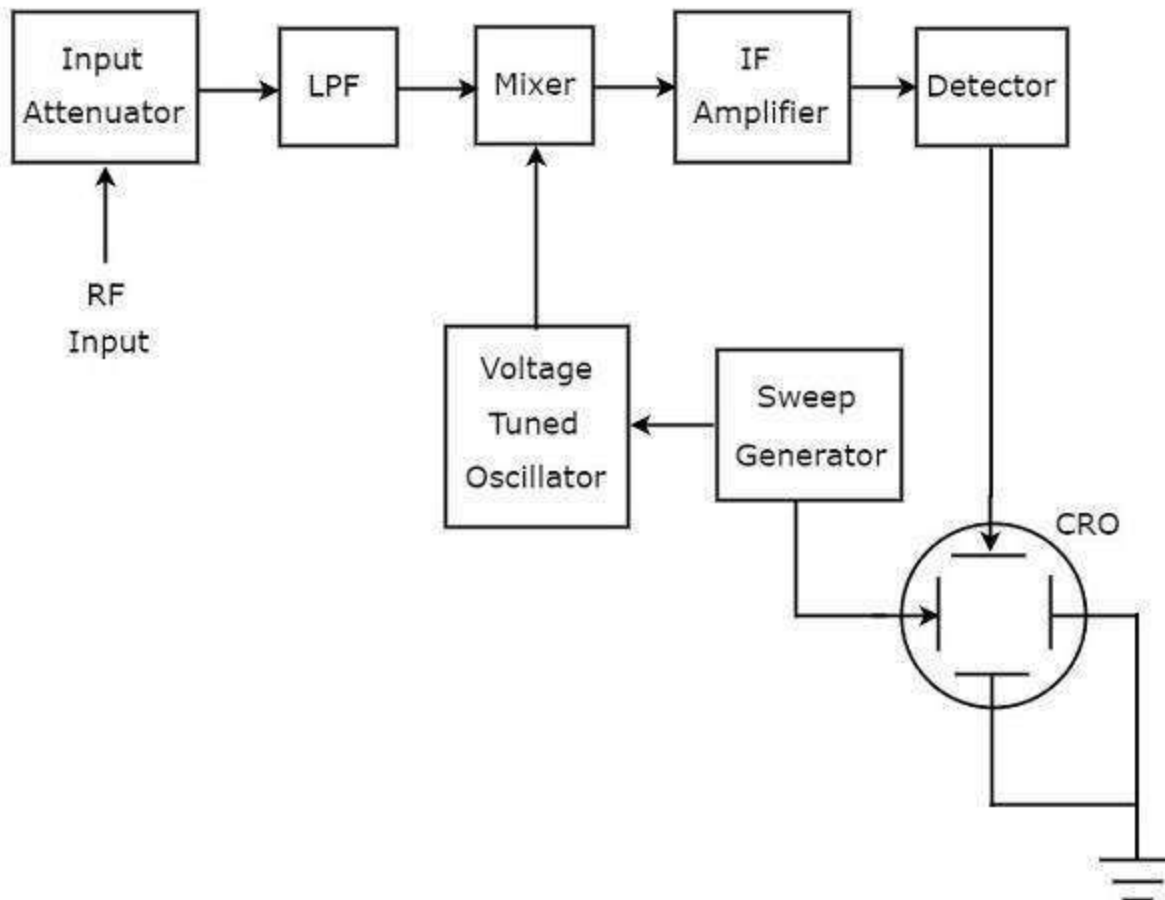The spectrum analyzer, used for analyzing the signals are of RF range is called **superheterodyne spectrum analyzer**. Its **block diagram** is shown in below figure



The **working** of superheterodyne spectrum analyzer is mentioned below.

- The RF signal, which is to be analyzed is applied to input attenuator. If the signal amplitude is too large, then it can be attenuated by an **input attenuator**.
- **Low Pass Filter** (LPF) allows only the frequency components that are less than the cut-off frequency.
- **Mixer** gets the inputs from Low pass filter and voltage tuned oscillator. It produces an output, which is the difference of frequencies of the two signals that are applied to it.
- **IF amplifier** amplifies the Intermediate Frequency (IF) signal, i.e. the output of mixer. The amplified IF signal is applied to detector. The output of detector is given to vertical deflection plate of CRO. So, CRO displays the frequency **spectrum of RF signal** on its CRT screen. So, we can choose a particular spectrum analyzer based on the frequency range of the signal that is to be analyzed.

Data Acquisition Systems(DAS):

The systems, used for data acquisition are known as **data acquisition systems**. These data acquisition systems will perform the tasks such as conversion of data, storage of data, transmission of data and processing of data.

Data acquisition systems consider the following **analog signals**.

- Analog signals, which are obtained from the direct measurement of electrical quantities such as DC & AC voltages, DC & AC currents, resistance and etc.
- Analog signals, which are obtained from transducers such as LVDT, Thermocouple & etc.

Types of Data Acquisition Systems:

Data acquisition systems can be classified into the following **two types**.

- Analog data acquisition system
- Digital Data Acquisition System

Analog Data Acquisition Systems:

The data acquisition systems, which can be operated with analog signals are known as **analog data acquisition systems**. Following are the blocks of analog data acquisition systems.

- **Transducer:** It converts physical quantities into electrical signals.
- **Signal conditioner:** It performs the functions like amplification and selection of desired portion of the signal.
- **Display device:** It displays the input signals for monitoring purpose.
- **Graphic recording instruments:** These can be used to make the record of input data permanently.
- **Magnetic tape instrumentation:** It is used for acquiring, storing & reproducing of input data.

Digital Data Acquisition Systems:

The data acquisition systems, which can be operated with digital signals are known as **digital data acquisition systems**. So, they use digital components for storing or displaying the information. Mainly, the following **operations** take place in digital data acquisition.

- Acquisition of analog signals
- Conversion of analog signals into digital signals or digital data
- Processing of digital signals or digital data

Following are the blocks of **Digital data acquisition systems**.

- **Transducer:** It converts physical quantities into electrical signals.
- **Signal conditioner:** It performs the functions like amplification and selection of desired portion of the signal.
- **Multiplexer:** It connects one of the multiple inputs to output. So, it acts as parallel to serial converter.

- **Analog to Digital Converter:** It converts the analog input into its equivalent digital output.

- **Display device:** It displays the data in digital format.

- **Digital Recorder:** It is used to record the data in digital format.

Data acquisition systems are being used in various applications such as biomedical and aerospace. So, we can choose either analog data acquisition systems or digital data acquisition systems based on the requirement.